

UNIT - I : CMOS PHYSICS, TRANSCIEVER SPECIFICATIONS AND ARCHITECTURES.

CMOS: Introduction to MOSFET physics - Noise: Thermal, shot, flicker, popcorn noise -

Transceiver specifications: Two port Noise theory, Noise figure, THD, IP2, IP3, sensitivity, SFDR - phase noise - Transceiver Architecture:

Receiver: Homodyne, Heterodyne, Image reject, Low - IF Architecture - Transmitter:

Direct-up conversion, Two-step up conversion schemes.

www.EnggTree.com.

MOSFET Physics - Introduction

A basic n-channel MOSFET consists of two heavily doped n-type regions, the source and drain that forms the main terminals of the device the gate is lightly doped. The substrate terminal is at the same potential as source. The substrate forms the fourth terminal whose influence cannot be ignored.


When positive voltage is applied at the gate holes are repelled away from the substrate. At some point of gate voltage (Threshold voltage)

V_t , the surface becomes charge depleted. Further increase in gate voltage under inversion layer of electrons supplied by source or drain that constitute a conductive path or channel between drain and source. When gate-source voltage is above V_t , the device is said to be in strong inversion.

with assumption of drain to zero voltage is zero, the induced inversion charge is proportional to the gate voltage above the threshold, and the induced charge density is constant along the channel.

If we apply a positive drain voltage V_d , the channel potential must increase from 0 at the source to V_d at drain end. The net voltage there to induce an inversion layer decreases when reaches the drain end of the channel.

 The induced channel charge density will vary from max at source to min at drain of the channel.



Thus the channel charge density be

$$Q_n(y) = -C_{ox} \{ [V_{gs} - V(y)] - V_t \}$$

where $Q_n(y)$ is the charge density at y Position

C_{ox} is ϵ_{ox}/t_{ox} .

$V(y)$ is channel potential at y Position

as we follow y -direction along the channel.

C_{ox} is capacitance per unit Area.

The negative sign implies the charges are made of electrons in NMOS.

www.EnggTree.com

DRAIN CURRENT IN LINEAR (TRIODE REGION)

The linear or triode region is defined as one in which V_{gs} is large enough for the formation of inversion layer from the distance from source to drain.

$$[V_{gs} - V(y)] - V_t = 0$$

The charge density becomes zero at drain at some voltage. Thus the boundary for triode region is

$$[V_{gs} - V_{ds}] - V_t = 0 \Rightarrow V_{gs} - V_t = V_{ds} \cong V_{dsat}$$

As long as $V_{ds} < V_{dsat}$, the device is in linear region of operation

The expression of the devices current in terms of variable

$$I_D = -WQ_n(y)v(y)$$

The velocity at low fields is simply the product of mobility and electric field

$$I_D = -WQ_n(y)\mu_n E$$

where W is width of device.

Substituting for charge density

$$I_D = -WCox[V_{gs} - V(y) - V_t]\mu_n E$$

The y directed electric field E is simply the gradient of voltage along the channel.

$$\therefore I_D = \mu_n Cox W [V_{gs} - V(y) - V_t] \frac{dV}{dy}$$

so that

$$I_D dy = \mu_n Cox W [V_{gs} - V(y) - V_t] dV$$

on integration

$$\int_0^L I_D dy = I_D L = \int_0^{V_{ds}} \mu_n Cox W [V_{gs} - V(y) - V_t] dV$$

\therefore The expression for drain current in triode region

$$I_D = \mu_n Cox \frac{W}{L} \left[(V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

Thus MOSFET in triode region behaves as voltage controlled resistor.

DRAIN CURRENT IN SATURATION

when V_{ds} is high, the inversion layer does not extend from source to drain so the channel is said to be 'pinched off'. In this condition, the field in channel charges increase causing total current to remain constant despite of increase in V_{ds} .

to calculate current easily substitute V_{dsat} for V_{ds} .

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_t) V_{dsat} - \frac{V_{dsat}^2}{2} \right]$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{gs} - V_t)^2$$

In saturation, the drain current has square independent on gate source voltage and is independent on drain voltage. As vacuum tube pentodes exhibit a similar insensitivity this regime is called the pentode region of operation.

The transconductance in saturation for drain current by differentiating be

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)$$

Also expressed as

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

with bipolar devices, a long channel MOSFET's transconductance depends on the square root of bias current.

CHANNEL - LENGTH MODULATION

So far we have assumed the drain current is independent of drain source voltage in saturation. The primary mechanism responsible for non-zero output conductance in long channel device is channel length modulation (CLM)

The drain current in both triode and saturation is

$$I_D = (1 + \lambda V_{ds}) I_{D0}$$

λ - Early voltage
 I_{D0} - I_D when CLM are ignored

OPERATION IN WEAK INVERSION

The MOSFET device conducts no current until inversion layer forms. The mobile carriers don't disappear the moment the gate voltage drops below V_t .

As V_{gs} drops below threshold the current decreases in exponential fashion much like BJT.

NOISE

The sensitivity of communication system is limited by noise. The fundamental noise source exist was identified in vacuum tube amplifiers. Engineers had access to gain to make the noise source. There were no improvement in further cascading amplifiers as a mysterious noise exists along with signal. In audio system this as continuous hiss while, in video as characteristic 'snow' of analog TV signals.

THERMAL NOISE

Thermally agitated charge carriers in a conductor has varying current that rises random voltage. Thermal noise is also called as Johnson noise, less frequency noise and Nyquist noise.

Due to noise in random, we cannot identify a specific value of voltage at any particular time and only way to identify the noise is by statistical measures like mean square or root mean square values. Due to thermal, there is dependence on absolute temperature, where the thermal noise power is exactly proportional to T . a quantity called available noise power and is given by


$$P_{NA} = kT\Delta f.$$

where k is Boltzmann's constant ($1.38 \times 10^{-23} \text{ J/K}$), T is absolute temperature in K , Δf is noise bandwidth in hertz.

The available noise power is ^{not} dependent of frequency and grows (ie) the total power grows as with bandwidth without limit.

The noise power over 1-Hz bandwidth is about $4 \times 10^{-21} \text{ W}$ (or -174 dBm)⁵ at room temperature. The noise power is same in interval between 1 MHz and 2 MHz to 1 GHz and 1.001 GHz as noise power is same over any bandwidth. Thermal noise is often called as 'white' by analogy with white light.

THERMAL NOISE OF RESISTOR

 


The noise voltage generator in series with resistor. The power delivered by this noisy resistor to another resistor of equal value is given by definition of available noise power

$$P_{NA} = kT\Delta f = \frac{e_n^2}{4R}$$


where e_n is the rms noise voltage generated by resistor R over band width Δf at given temperature. The mean square open circuit noise voltage is given by $\overline{e_n^2} = 4KTR\Delta f$.

At room temperature a $1k\Omega$ resistor generates $4nV$ of rms noise over bandwidth of $1Hz$, while 50Ω generates $0.9nV$ of rms noise over same bandwidth.

RESISTOR THERMAL NOISE MODELS

 

$$\overline{e_n^2} = 4KTR\Delta f$$

 

$$i_n^2 = \frac{\overline{e_n^2}}{R^2} = \frac{4KTR\Delta f}{R}$$

$$= 4KT\Delta f$$

The noise bandwidth is

$$\Delta f \equiv \frac{1}{|H_{PK}|^2} \int_0^\infty |H(f)|^2 df$$

H_{PK} is peak value of magnitude of filter voltage transfer function $H(f)$

For a single pole RC low pass filter the -3-dB bandwidth (hertz) is simply $1/2\pi RC$, but the equivalent noise bandwidth is as

$$\Delta f = \frac{1}{11^2} \int_0^\infty \left[\frac{1}{(2\pi RC f)^2 + 1} \right] df$$

$$= \frac{1}{2\pi RC} \int_0^\infty \arctan 2\pi f RC \Big|_0^\infty$$

$$= \frac{\pi}{2} f_{3dB} = \frac{1}{4RC}$$

The single pole LPF has noise bandwidth is about 1.57 times the -3-dB bandwidth.

Similarly calculation shows that a critically damped second order LPF has noise bandwidth is about 1.22 times the -3-dB bandwidth.

A more general expression for the thermal noise voltage is as

$$E_n^2 = \frac{h\nu R \Delta f}{\pi} \coth \left(\frac{h\nu}{4\pi kT} \right)$$

h is plank's constant which is 6.62×10^{-34} J-s

THERMAL NOISE IN MOSFET

Both BJT and MOSFET are voltage controlled resistors, they exhibit thermal noise. In triode region, practically there will be noise with resistance value

The expression for drain current noise in FETs

$$i_{nd}^2 = 4kT \gamma g_{do} \Delta f$$

where g_{do} is drain source conductance at zero V_{ds} . The parameter γ has value of unity at zero V_{ds} , in long devices, decrease toward a value of $2/3$ in saturation


In some cases shows that short channel NMOS devices exhibit more in excess of values predicted by long channel theory.

SUBSTRATE THERMAL NOISE

The thermal noise associated with the substrate resistance can produce measurable effect at main terminal of devices

The thermal noise R_{sub} modulate the potential of back gate contributing noise drain current
 
$$i_{nd,sub}^2 = 4kTR_{sub} g_{mb} \Delta f$$



Depending on bias condition and also on magnitude of substrate resistance and size of back gate transconductance the noise generated is often called epi noise.


The physical structure and corresponding frequency-dependent expression is for substrate noise is

$$I_{ndsub}^2 = \frac{4KT R_{sub} g_m^2 \Delta f}{1 + (WR_{sub} C_{cb})^2}$$

GATE NOISE

In addition to thermal noise, aguation of channel charge has other outcome: gate noise. The floating channel potential couples capacitively into gate terminal leading to noisy gate current. Vander Ziel's expression gate noise

 is as $I_{ng}^2 = 4KT S g g \Delta f$
 $g g = \frac{\omega^2 C_g^2}{5g_{do}}$



The gate noise current has a spectral density that is not constant and increases with frequency and is called 'blue noise' to continue the optical energy.

The alternative gate noise is given by

$$I_{ng}^2 = \frac{1}{g g} \cdot \frac{1}{Q^2 + 1} \approx \frac{1}{g} \cdot \frac{Q}{Q^2} = \frac{1}{5g_{do}}$$

SHOT NOISE

Shot noise was explained by Schottky in 1918 and occasionally known as Schottky noise, which is granular nature of electronic charge. Two conditions for shot noise to occur.

The term $1/f$ suggests, the noise is characterized by a spectral density that increases without time limit as frequency decreases. Due to lack of unifying theory, the mathematical expression for $1/f$ noise contain various Empirical Parameters as below

$$\bar{N}^2 = \frac{k}{f^n} \Delta f$$

\bar{N} is rms noise (either Voltage or current).

k is empirical Parameter.

The parameter n is occurring at value of unity, on integration the density to find noise in frequency band bounded by lower frequency f_1 and upper frequency f_2 is given by

$$\bar{N}^2 = \int_{f_1}^{f_2} \frac{k \cdot df}{f} = k \ln\left(\frac{f_2}{f_1}\right)$$

which says the total mean-square noise depends on the log of the frequency ratio.

FLICKER NOISE IN RESISTOR

The noise in resistor is often called excess noise as this noise is in addition to what is expected from thermal noise

- (i) There must be direct current flow and also a potential barrier over which the charge carriers hop.
- (ii) Ordinary, linear resistors do not generate shot noise despite of quantized nature of electronic charge.

The shot noise is given by.

$$\bar{i}_n^2 = 2q I_{DC} \Delta f$$

\bar{i}_n^2 - rms of noise current

q - quantum electronic charge ($1.6 \times 10^{-19} C$)

I_{DC} - DC current in A.

Δf - noise bandwidth in Hertz.

The shot is not corruption of 'Schottky' on connection of audio system with a source of shot noise biased at very low current, the resulting sound is much like that of duck shot (pellets) dropping onto a hard surface.

FLICKER NOISE

The mysterious type of noise is flicker noise, also known as $1/f$ noise or pink ²⁰ noise.

Carbon film resistors exhibit less noise than carbon composition types. It is true that excess noise increases with DC, so one must minimize DC drop across a resistor.

$$\overline{i_n^2} = \frac{k}{f} \cdot \frac{R_D^2}{A} \cdot V^2 \Delta f$$

A is Area of resistor

R_D is sheet resistivity

V is the Voltage across resistor, k is material specific parameter.

FLICKER NOISE IN MOSFET

In electronic devices, $1/f$ noise arises from a number of different mechanisms and it is most significant in MOSFET than in bipolar devices as MOSFET devices are surface devices, they exhibit this type of noise to a much greater degree than bipolar. Larger MOSFETs exhibit less $1/f$ noise because of their large gate capacitance smoothes the fluctuations at channel charge.

The mean-square $1/f$ drain noise current is given by

$$\overline{i_n^2} = \frac{k}{f} \cdot \frac{g_m^2}{WLC^2 \alpha} \cdot \Delta f$$

$$\approx \frac{k}{f} \cdot W^2 T \cdot A \cdot \Delta f$$

where A - area of gate and k is device-specific constant. Thus for a fixed transconductance, a larger gate area and thinner dielectric reduce this noise term.

FLICKER NOISE IN JUNCTIONS

Forward-biased junctions also exhibit $1/f$ noise. The noise is proportional to the bias current and inversely proportional to junction Area.

$$\overline{i_n^2} = \frac{k}{f} \cdot \frac{I}{A_j} \cdot \Delta f$$

k is constant and value of around $10^{-25} A^{-1} m^2$.

POPCORN NOISE


Another type noise in semiconductor is known as Popcorn noise, Also known as burst noise, bistable noise, random telegraph signals (RTS)

Gold plated BJT exhibit highest level of burst noise and may be very sensitive to contamination by metal ions.

This noise was observed in point-contact diode, ordinary junction diode and tunnel diode, resistor of some type and both discrete and integrated circuit junction transistor.

The equation is
 
$$\overline{N^2} = \frac{k}{1 + (f/f_c)^2} \Delta f$$



k is empirical value.

f_c is corner frequency

For frequency below f_c , the current noise density flattens out.

for frequency well above f_c , the

total mean square noise between f_1 and

f_h is

$$k_2 f_c^2 \left[\frac{1}{f_1} - \frac{1}{f_h} \right]$$


TRANSDUCER SPECIFICATIONS:

TWO PORT NOISE THEORY

NOISE FACTOR

A useful measure of the noise performance of a system is the noise factor denoted by F

to optimize noise performance in c/s

 

A noisy two port driven by source with admittance Y_s and equivalent shunt noise current I_n we are concerned only with over all input-output behaviour and unnecessary to track of all internal noise sources and the net effect of all noise sources can be represented by one pair of external sources: - a noise voltage and noise current.

The noise factor is defined by

$$F \equiv \frac{\text{total output noise power}}{\text{output noise due to input source}}$$

By convention, the source is at a temperature of 290K. The noise factor is a measure of degradation in signal-to-noise ratio that system introduces. The larger the degradation, the larger the noise factor. If a system adds no noise of its own, the total output noise is due to source only and noise factor is unity.

An equivalent method is to compute the total short-circuit mean square noise current and then divide the total by short circuit mean square current due to input source. In this the power contributions are proportional to short circuit mean square current with proportionality constant.

While using this we may encounter the problem of combining noise sources that are varying in degree of correlation with each other.

In this special case of zero correlation the expression for noise figure is

$$F = \frac{|i_n|^2 + |i_c + i_u|^2}{|i_n|^2} \quad \text{--- (1)}$$

For correlation between e_n and i_n make i_n as sum of two components. one i_c is correlated and with e_n and other i_u is not correlated.

$$i_n = i_c + i_u \quad \text{--- (2)}$$

Since i_c is correlated with e_n

$$i_c = \gamma_c e_n \quad \text{--- (3)}$$

γ_c is correlation admittance

Combining (1), (2) and (3)

The factor becomes

$$F = \frac{|i_n|^2 + |i_u + (\gamma_c + \gamma_s) e_n|^2}{|i_n|^2}$$

$$= 1 + \frac{|i_u|^2}{|i_n|^2} + |\gamma_c + \gamma_s|^2 \frac{|e_n|^2}{|i_n|^2} \quad \text{--- (4)}$$

eqn (4) contains three independent noise sources, each is treated as thermal noise produced by equivalent resistance or conductance.

$$R_n \equiv \frac{|e_n|^2}{4KT\Delta f} \quad \text{--- (5)}$$

$$G_{iu} \equiv \frac{|i_u|^2}{4KT\Delta f} \quad \text{--- (6)}$$

$$G_s \equiv \frac{|i_s|^2}{4KT\Delta f} \quad \text{--- (7)}$$

using these equivalences, the expression for noise factor is written in terms of as impedance and admittance

$$F = 1 + G_{iu} + |\gamma_c + \gamma_s|^2 R_n$$

$$= 1 + G_{iu} + \frac{G_s}{G_c + G_s} \frac{R_n}{B_c + B_s} \quad \text{--- (8)}$$

Here each admittance into sum of conductance G and susceptance B .

OPTIMUM SOURCE ADMITTANCE

Once two port noise is given by four noise parameters G_c, B_c, R_n and G_u eqn (8) given condition for minimizing noise factor with fixed admittance into respect of source admittance with zero set.

NOISE FIGURE

other than noise factor, the other figure of merit is noise figure and noise temperature

The Noise Figure (NF) is the noise factor expressed in decibels

Noise Temperature T_N is an alternative way of expressing the effect of an amplifier's noise contribution and defined as the increase in temperature required of the source resistant for it to account for all of the output noise at reference temperature T_{ref} (290K).

$$F = 1 + \frac{T_N}{T_{ref}} \Rightarrow T_N = T_{ref} \cdot (F-1)$$

An amplifier that adds no noise of its own has a noise temperature of 0K.

Noise Temperature is useful for describing the performance of cascaded amplifiers whose noise factor is close to unity

IHD - Total Harmonic Distortion

-HARMONIC DISTORTION

The harmonic distortion RF circuits are due to non linearities

sum adm

$$B_s = -B_c = B_{opt}$$

$$G_s = \sqrt{\frac{G_u}{R_n} + G_c^2} = G_{opt}$$

To minimize the noise factor, the source susceptance should be made equal to the inverse of correlation susceptance, while source conductance should be set to value in G_{opt} .

$$F_{min} = 1 + 2R_n [G_{opt} + G_c] \\ = 1 + 2R_n \left[\sqrt{\frac{G_u}{R_n} + G_c^2} + G_c \right]$$

We may express noise factor in terms of F_{min} and source admittance

$$F = F_{min} + \frac{R_n}{G_s} \left[(G_s - G_{opt})^2 + (B_s - B_{opt})^2 \right]$$

Thus contours of constant noise factor are non-overlapping circles in admittance plane.

LIMITATIONS OF CLASSICAL NOISE OPTIMIZATION.

In RF design, the freedom to choose I_c relation there is no specific guidance is given that what device size will reduce noise.

Power consumption is not considered in classical noise optimization.

3rd order polynomial.

$$V_o(t) = \alpha_0 + \alpha_1 V_i(t) + \alpha_2 V_i^2(t) + \alpha_3 V_i^3(t)$$

$V_o(t)$ is output of amplifier

$V_i(t)$ is input voltage to the amplifier.

Generally a two tone test is used to compute IP3 for

$$V_i = A_{i1} \cos(\omega_1 t + \phi_1) + A_{i2} \cos(\omega_2 t + \phi_2)$$

$$\phi_1 = \omega_1 t + \phi_1$$

$$\phi_2 = \omega_2 t + \phi_2$$

substituting eqn ② in ①

$$V_o = \alpha_0 + \alpha_1 \left(\frac{3}{4} A_{i1}^2 + \frac{3}{2} A_{i1} A_{i2} \right) A_{i1} \cos \omega_1 t + \alpha_2 \left(\frac{3}{4} A_{i1}^2 + \frac{3}{2} A_{i1} A_{i2} \right)$$

fundamental.

$$+ \frac{1}{2} \alpha_2 (A_{i1}^2 \cos 2\omega_1 + A_{i2}^2 \cos 2\omega_2)$$

2nd harmonic.

At second order IP2 = second order IMD2

$$\left(\alpha_1 + \alpha_2 \left(\frac{3}{4} A_{i1}^2 \right) \right) A_{i1} = \frac{1}{2} \alpha_2 A_{i1} A_{i2}$$

$$\alpha_1 A_{i1} \approx \frac{1}{2} \alpha_2 A_{i1} A_{i2}$$

2nd order intermod component in output voltage

$$\frac{V_{o,1}}{V_{o,IMD2}} = \frac{\alpha_1 A_{i1}^2}{\frac{1}{2} \alpha_2 A_{i1} A_{i2}} = \frac{A_{i1}^2}{A_{i1} A_{i2}}$$

sinusoid is applied to non-linear

system, the output exhibit frequency

components that are unrelatd to input

$\omega =$ fundamental frequency

$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t +$$

$$\alpha_3 A^3 \cos^3 \omega t$$

$$x(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$x(t) = y(t) = \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} (3 + \cos 2\omega t + \cos 3\omega t)$$

$$\alpha_1 A \cos \omega t + \frac{2}{3} \alpha_2 A^3 (3 + \cos 2\omega t + \cos 3\omega t)$$

$$\alpha_1 A \cos \omega t + \alpha_2 A^2 \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t$$

$$+ \frac{\alpha_2 A^2}{2} \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t$$

operated with harmonic bandpass

SECOND INTERCEPT POINT IP2

IP2 is also known as SOI, 1IP2

is a measure of linearity that quantifies the second order distortions generated

by non-linear system and devices.

It is an interpotated point, where the fundamental component power curve

meets the second order intermod (IMD2)

Consider non linear amplifier whose output to output characteristics is given by

SENSITIVITY

which is defined as the minimum signal level that a receiver can detect with the acceptable quality. In presence of more noise, the detected signal becomes unintelligible and carries little information.

SNR in range of 6 to 25 dB.

sensitivity can be written as

$$NF = \frac{SNR_{in}}{SNR_{out}}$$

$$= \frac{P_{sig}/P_{rs}}{SNR_{out}}$$

P_{sig} - input signal power and
 P_{rs} - source resistance noise power.

$$P_{sig} = P_{rs} \cdot NF \cdot SNR_{out}$$

To obtain total mean squared power.

$$P_{sig, tot} = P_{rs} \cdot NF \cdot SNR_{out} \cdot B$$

$$P_{sen} \text{ dBm} = P_{rs} \text{ dBm} + 10 \log B + SNR_{min} \text{ dB} + 10 \log B$$

P_{sen} is sensitivity and B in Hz is directly depend on gain of the system. antenna $P_{rs} = kT = -174 \text{ dBm/Hz}$. If receiver is matched to antenna.

$$P_{sen} = -174 \text{ dBm/Hz} + NF + 10 \log B + SNR_{min}$$

THIRD INTERCEPT POINT

The concept of IP3 originates from observation of amplitude of each tone rises that of output IM products increase more sharply at αA^3 . if we raise amplitude of IM products become equal to fundamental tones at output.


To find IIP3

$$|\alpha_1 A_{IIP3}| = \left| \frac{3}{4} \alpha_3 A_{IIP3}^3 \right|$$

$$A_{IIP3} = \sqrt{\frac{4}{3} \left| \frac{\alpha_1}{\alpha_3} \right|}$$


$$\frac{A_{IIP3}}{A_{1dB}} = \sqrt{\frac{14}{0.435}}$$

$$\approx 9.6 \text{ dB}$$

 

PHASE NOISE

 An ideal oscillator produces perfectly-periodic output of the form $x(t) = A \cos \omega_c t$. The zero crossing occurs at exact integer multiples of $T_c = 2\pi/\omega_c$.




$$x(t) = A \cos[\omega_c t + \phi_n(t)]$$

$$\approx A \cos \omega_c t - A \sin \omega_c t \sin[\phi_n(t)]$$

$$\approx A \cos \omega_c t - A \phi_n(t) \sin \omega_c t$$

EFFECT OF PHASE NOISE

 


TRANSCEIVER ARCHITECTURE

There are 2 main architecture and RF receiver of any sim. They are.

- (i) Heterodyne
 - (ii) Homodyne
- where both converts modulated RF signal to baseband I/Q signal zero IF frequency.


HETERODYNE RECEIVER

 

It requires one mixer to bring the modulated RF signal to modulated IF signal, which is applied to I/Q demodulator which brings the modulated low IF to baseband at zero IF.


HOMODYNE RECEIVER

 In homodyne receiver, it does not require any mixers at RF stage. The modulated RF signal is directly applied to I/Q demodulator which gives base band signals out (I and Q) at zero F.



This I/Q demodulator circuit which is used in all moderns that converts the modulated IF/RF signal to baseband signal at zero frequency. To frequency is chosen.

$\omega_0 = 2\pi f_0$

 

The signal is first amplified at low noise stage known as LNA. After the low noise amplification signal is converted to base band. If RF frequency signal and LO frequency signal are equal the circuit operates as a phase detector.

IMAGE REJECTION RECEIVER

Image reject architecture are another class of receivers that suppress the image without filtering it by avoiding the trade off between the image rejection and channel selection.

Define 90 degree phase shift.

$$A \cos(\omega_c t - 90^\circ) = \frac{A}{2} e^{+j\omega_c t} + \frac{A}{2} e^{-j\omega_c t} = A \sin \omega_c t$$


Similarly in narrow band modulated signal $x(t) = A(t) \cos[\omega_c t + \phi(t)]$ we do 90 degree phase shift.

$$A(t) \cos[\omega_c t + \phi(t) - 90^\circ] = A(t) \frac{e^{+j(\omega_c t + \phi(t) - 90^\circ)} + e^{-j(\omega_c t + \phi(t) - 90^\circ)}}{2} = A(t) \sin[\omega_c t + \phi(t)]$$

$$X_{90}(w) = X(w) [-j \operatorname{sgn}(w)]$$

where $\operatorname{sgn}(w)$ is sign function
 This shift by 90° is called Hilbert transform which negates the original signal.

LOW IF RECEIVER ARCHITECTURE

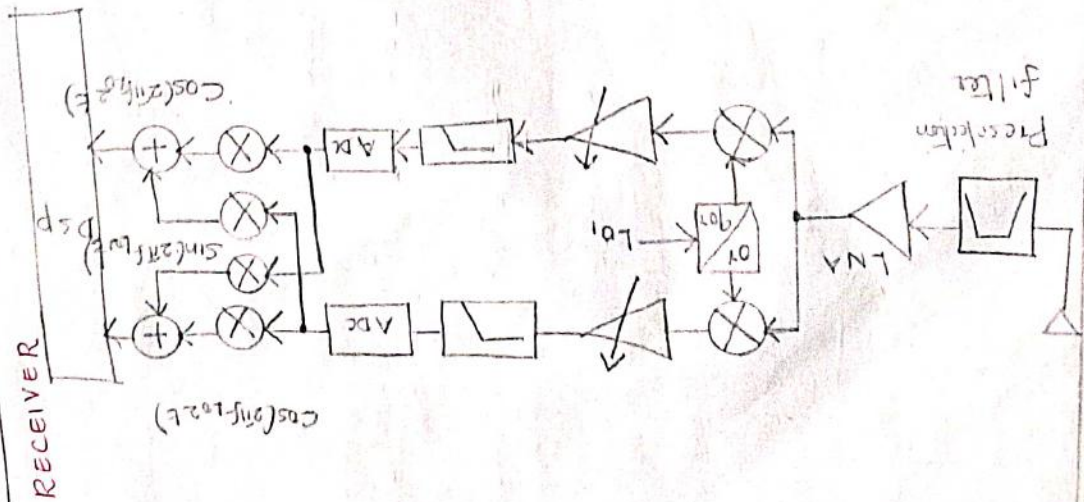

At the hybrid out:

$$V_{OL,I} = V_{OL} \cos(\omega_0 t)$$

$$V_{OL,Q} = -V_{OL} \sin(\omega_0 t)$$

At the mixer out:

$$V_U = -K V_{OL} V_M \cos(\omega_0 t + \phi) \sin(\omega_0 t)$$

$$= \frac{1}{2} K V_{OL} V_M (\cos(2\omega_0 t + \phi) + \sin(\phi))$$

$$V_L = K V_{OL} V_M \cos(\omega_0 t + \phi) \cos(\omega_0 t)$$

$$= \frac{1}{2} K V_{OL} V_M (\cos(2\omega_0 t + \phi) + \cos(\phi))$$

The low Pass (LP) filter removes the component at $2\omega_0$ (and all the others produced by the actual non-linearities). The output of two signals are then proportional to I and Q components of the modulated R.F signal.

Pros & cons.

- * Reduced complexity
- * Easier to integrate
- * More susceptible to noise and distortion.
- * DC offset voltage at the mixer output due to spurious signal from antennas

* * Offset voltage at mixer output not easy to eliminate


TRANSMITTER ARCHITECTURE.

The choice of Transmitter is determined by 2 factor.

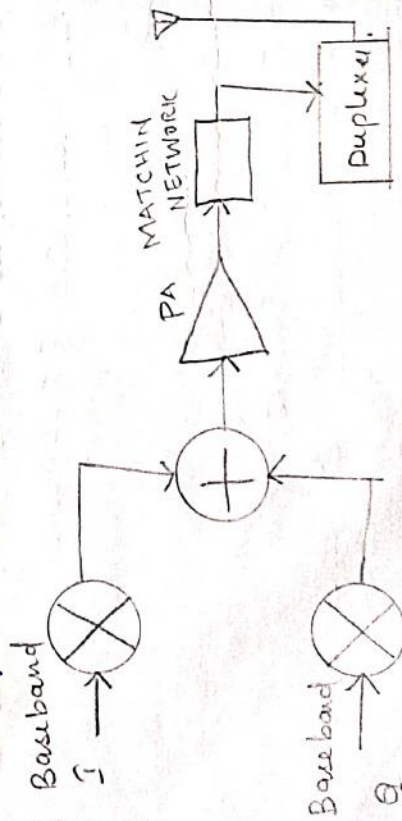- (i) wanted and unwanted emission requirements
- (ii) no of oscillators and external filters.


DIRECT UP CONVERSION ARCHITECTURE.

In direct conversion architecture transmits the output carrier frequency is equal to the LO frequency and modulation, up conversion occur in the same circuit. The topology simplicity makes for high level of integration.



The direct - conversion draws back

 - * Disturbance of the local oscillator by the power amplifier output. This issue arises because the PA output is a modulated waveform having a high power and a spectrum centered around the LO frequency




DIRECT UP CONVERSION TRANSMITTER

TWO-STEP ARCHITECTURE

Another approach to circumventing the problem of LO pulling in Transmitters is to upconvert the baseband signal - two or more steps so that the PA output spectrum is far from the frequency of the VCO's.

TWO STEP TRANSMITTER.

 

The channels baseband I and Q undergo quadrature modulation at a lower frequency ω_1 [called the intermediate frequency (IF)] and the result is upconverted to $\omega_1 + \omega_c$ by mixing the band pass filtering. The first BPF suppresses the harmonics of the IF signal while the second removes the unwanted sideband centered around $\omega_1 - \omega_c$.

Advantages.
Over the direct approach is that using quadrature modulation is performed at lower frequencies I and Q matching is superior leading to less cross-talk between two bit streams.
A channel filter may be used at the first IF to limit the transmitted noise and spurs in adjacent channels.

The difficulty in two-step transmitters is that the bandpass filter following the second upconversion must reject the unwanted side band by large factor typically 50 to 60 dB. This is because the simple upconversion operation produces both the wanted and the unwanted side bands with equal magnitude. Owing to higher center frequency, this filter is typically a passive, relatively expensive off-chip device.

SPURIOUS FREE DYNAMIC RANGE (SFDR)

Another popular specification in communication system is spurious free dynamic range.

The two variations

(i) single-tone SFDR

is the ratio of signal to the most spur in the band width of interest which is not harmonic and can be referenced to the signal or carrier level (dBc) or to full scale (dBFS)

TWO Marks

1. Can MOSFET conduct in both directions
Yes, MOSFET are bi-directional
2. What are the types of MOSFET and regions of operations?
Types.

- * Enhancement mode
- * Depletion mode

Region of operations

- (i) cut-off region
- (ii) Linear region
- (iii) saturation region

3. List the effects of non-linearity in amplifiers.

The effects of non-linearity in amplifiers are

- (i) Harmonic Distortion
- (ii) intermodulation Distortion
- (iii) Phase noise
- (iv) Other noise: Thermal, Popcorn noise, Flicker noise and etc.


The reference is minimum detectable signal level at the input of a receiver which can be calculated with noise figure and input signal bandwidth of the receiver. The difference between this value and the input products which will produce detectable signal is equal to minimum detectable signal referred as ITB the input of the system is SFDR. This procedure for ADC.

$$DRF(dB) = \frac{2}{3} (P_3 - N_0)$$

P_3 - third order intercept point

N_0 - is noise component (dB/dBm).

www.EnggTree.com

 

4. What are the choice of substrate material in amplifiers.

- * Most widely used is its excellent material is silicon, due to its excellent semiconductor properties, low cost and high integration density.

5. Derive expression for phase noise

$$\begin{aligned}
 x(t) &= A \cos(\omega_c t + \phi_n(t)) \\
 &\approx A \cos \omega_c t - A \sin \omega_c t \sin(\phi_n(t)) \\
 &\approx A \cos \omega_c t - A \phi_n(t) \sin \omega_c t.
 \end{aligned}$$

6. What is Noise Figure

Noise figure is the noise factor expressed in decibels. usually the difference between the decibels of noise output of the actual (receiver) to the ideal (receiver) with same over all gain and band width matched to sources at stand noise temperature (290K).

7. What is image rejection
Image rejection is the measure of the receiver's ability to reject the signals at image frequency. normally in dB.


8. What are the Draw backs of Direct conversion Receivers.

- * DC offset - is coming from local oscillator leakage cause large DC offset in the baseband
- * There is a small voltage in the local oscillator and find a way as input of LNA, through mixer due to poor isolation. Even, there is isolation we will have small leakage as it is not possible to eliminate completely.

UNIT II : IMPEDENCE MATCHING NETWORKS AND AMPLIFIERS.


Review of S-parameters and Smith chart - Passive IC components - impedance matching networks - Amplifiers: common Gate, common source Amplifiers - OC time constants in bandwidth estimation and enhancement - high-frequency amplifier design - Low noise Amplifiers: Power match and noise Match, single-ended and differential LNAs.

REVIEW OF S-PARAMETERS.

 


S-parameters are useful method for representing a circuit as 'Black box'. The external behaviour of this black box can be predicted without any regard for the contents. This black box can be

 - * A resistor
- * a transmission line or
- * a integrated circuit



 This is a simple network with 2 ports. A port is Terminal pair of lines. S-Parameters are measured by sending a single frequency signal into the network and to detect what waves exit from each port.




Power, Voltage, current are travelling waves in both direction. The wave incident on port 1, some of the signal reflects back and some exit other port. S_{11} refers to reflected at port 1 for signal incident at port 1. * S-Parameter S_{11} is ratio of two waves b1/a1. S_{21} refers to exiting at port 2 for incident at Port 1. * S-Parameter S_{21} is ratio of two waves b2/a1. (S_{21} is considered of S_{12} -> because responding Port is always first considered).

S-Parameters are complex (ie they have magnitude and angle because both Magnitude and Phase of input signal are changed by network and thus referred as complex scattering Parameters).
 These 4 S-Parameters actually contain eight separate numbers, i.e. the real and imaginary parts.

S-PARAMETERS DEPEND ON

S-Parameters depend on the network and the characteristic impedance of the source and load used to measure it, and frequency measured at.

(ie)

 

- The S-Parameters change
- (i) when network change
- (ii) when frequency is changed
- (iii) when load impedance is changed
- (iv) when source impedance is changed.

MATRIX ALGEBRAIC REPRESENTATION OF 2-PORT S-PARAMETERS:

$$b_1 = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \times \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

S_{11} is reflection coefficient (they refer to the reflection occur at port 1 only)

S_{21} is transmission coefficient from one port to another port


Some matrices are symmetrical about diagonal. In 2 port network of symmetrical means $S_{21} = S_{12}$ and interchanging input and output port does not change transmission properties.

EXAMPLE OF 2-PORT SYMMETRICAL NETWORK IS A TRANSMISSION LINE



S_{21} refers to signal entering at port 1 and exiting at port 2.

S-Parameter - ratio of waves b_2/a_1

 

S_{22} is signal entering at port 2 for port 2 terminated signal. S_{22} is ratio of b_2/a_2

A linear network characterised by a set of simultaneous eqn describing existing from each port in terms of incident waves.

$$S_{11} = b_1/a_1$$

$$S_{12} = b_1/a_2$$

$$S_{21} = b_2/a_1$$

$$S_{22} = b_2/a_2$$

The transmitted and reflected wave will have change in amplitude and phase from incident wave. Generally reflected wave will be at same frequency as incident wave.

SMITH CHART:

The reflection co-efficient Γ is given in terms of normalized load impedance.

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \quad \text{--- (1)}$$

REASONS FOR GOING TO SMITH CHARTS.

Smith chart is more straight forward to plot the real and imaginary parts of impedance directly in standard cartesian co-ordinates.

* Because, plotting infinite impedance directly creates practical problems, and plotting in Γ handles impedance neatly as it cannot exceed unity for passive loads.

* Γ repeats every half-wavelength, when a lossless transmission line is terminated in a fixed impedance.

Eqn (1) is mapping of one complex number to another, so bilinear transformation is used, which is the ratio of two linear functions, because circles remain as circles when mapped and lines are considered as circles of infinite radius.

Hence circles and lines map into either circles or lines.

From Eqn (1), Γ is straight forward to


LARGER NETWORKS.

A network may have any number of ports.

* The S-matrix of an n-port contains n^2 coefficients (S-Parameters), each one representing a possible input-output path.

* The number of rows and columns in an S-parameter matrix is equal to the number of ports.

 * S-parameter subscripts 'ij'. 'j' is port that is excited (input port) and 'i' is the output port.




$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \times \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{bmatrix}$$

* The bottom half of Z-plane maps into the bottom half of unit circle in Γ -plane and thus capacitive impedance are found there.

* IIIly the top half of Z-plane corresponds to the top half of unit circle and inductive impedance.

* The smaller circles of constant resistance correspond to progressively larger resistance values.

 The point $\Gamma = -1$ corresponds to $Z=0$ and the point $\Gamma = 1$ corresponds to infinite resistance (or) reactance.



VSWR - Voltage Standing Wave Ratio


* is ratio between transmitted and reflected Voltage Standing wave in RF transmission system.

* measures how RF power is transmitted from power source through transmission line to the load

to show imaginary axis of Z-plane maps into the unit circle of Γ -plane, while the other constant-resistance, that maps to circles of varying diameter, that all are tangent at point $\Gamma = -1$.

Lines of constant reactance are orthogonal to lines of constant resistance in Z-plane sense, which maps to lines or circles, we expect constant reactance line to transform to the circular arcs.

 The smith chart is just plotting of both constant-resistance and constant-reactance contours in Γ -Plane without any explicit presence of Γ -Plane axes. The center of smith chart corresponds to zero reflection coefficient and therefore, a resistance equal to the normalizing impedance.




PASSIVE IC COMPONENTS

PARALLEL RLC TANK:-

This circuit exhibits Resonant behaviour
This circuit is often called as Tank circuit or simply tank.

 We begin by studying its complex impedance or more directly its admittance (for parallel network) $Y = G + jB$



At low frequency, the network admittance is essentially that of inductor and capacitor at very high frequency $X_L = X_C$

The Resonant frequency is given by

$$\frac{1}{\sqrt{R^2 + (\frac{1}{\omega C} - \frac{1}{\omega L})^2}} = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0 = \frac{1}{\sqrt{LC}}$ (impedance) $f_0 = \frac{1}{2\pi\sqrt{LC}}$ (Resonant)

QUALITY FACTOR:

$Q = \omega_0 L = \frac{\text{Energy stored}}{\text{Average Power dissipated}}$
 $\omega_0 = \frac{1}{\sqrt{LC}}$
 At Resonant frequency the energy in network moves back and forth between the inductor and capacitor with a constant sum at resonance.

Network Energy and power is given by

$E_{avg} = \frac{1}{2} C (I_{PK} R)^2$ $V = IR$
 Band width \downarrow \uparrow Band width
 spurs \downarrow \uparrow spurs
 Q is given by $Q = \omega_0 \frac{E_{W}}{P_{avg}} = \frac{1}{\frac{1}{Q} C (I_{PK} R)^2} = \frac{1}{\frac{1}{2} I_{PK}^2 R}$
 resonance
 $= \frac{R}{\sqrt{L/C}}$, where $\sqrt{L/C}$ is characteristic impedance

SERIES RLC NETWORK.


The equation for Q involves the same terms as for parallel case. The reciprocal form

$Q = \sqrt{L/C}$
 R

At resonance, the voltage across either the inductor or capacitor is Q times as great as that resistor.


OTHER RESONANT RLC NETWORKS:

 Pure parallel or series RLC network rarely exist so we will consider a realistic example.



THE MAXIMUM POWER TRANSFER THEOREM

We will consider the below example

 


X_s - fixed source impedance, Z_L - maximize the power deliver to the load

The power delivered to the load impedance is entirely due to R_L , as reactive elements do not dissipate power and power is simply delivered.

$$\frac{|V_R|^2}{R_L} = \frac{R_L [V_s]^2}{(R_L + R_s)^2 + (X_L + X_s)^2}$$

To maximize the power delivered to R_L i.e. X_L and X_s should be same and their to zero. and hence the maximum power transfer from a fixed source impedance to load occurs, when the load and source impedance are complex conjugate

 For practical methods to achieve maximum power transfer by



$$\frac{(w_0 I_p)^2 R_p + j w_0 I_p R_p}{R_p^2 + (w_0 I_p)^2}$$

$$j w_0 L_s + R_s = [j w_0 L_p || R_p]$$

If we equal real and $Q = R_p / w_0 L_p = w_0 L_s / R_s$
 $R_p = R_s (Q^2 + 1)$

equating imaginary
 $L_p = L_s \left(\frac{Q^2 + 1}{Q^2} \right)$

Similarly eqn for computing series and

Parallel RC equivalent:

$$R_p = R_s (Q^2 + 1)$$

$$C_p = C_s \left(\frac{Q^2}{Q^2 + 1} \right)$$

$$R_p = R_s (Q^2 + 1)$$


$$X_p = X_s \left(\frac{Q^2 + 1}{Q^2} \right)$$

This way, we need to remember a

single piece of universal formulas in order to convert any RLC network to pure parallel / series.

RLC NETWORK AS IMPEDENCE TRANSFORMER

 Circuit design at low frequency usually proceed in ignorance of the Max power transfer theorem derived.



Q in right network = $\frac{\omega L_2}{R_1}$
 $= \sqrt{\frac{R_P}{R_1} - 1}$
 $= \text{ought}$

Q in left network = $\frac{\omega(L_1 + L_2)}{R_1}$
 $= \sqrt{\frac{R_P}{R_1} - 1 + \frac{R_P}{R_1}}$

The above eqn allows us to find the image resistance, once R is computed the total inductance is found

The capacitance
 $C_1 = \frac{Q \text{ left}}{\omega R_{in}}$
 $C_2 = \frac{Q \text{ right}}{\omega R_P}$
 $R_1 = \frac{(\sqrt{R_{in}} + \sqrt{R_P})^2}{Q^2}$

R_s is load resistance, when this resistor is viewed across capacitor. It is transformed to equivalent. This is called L-match, because of its shape and simplicity as there are only two degree of freedom. (i) impedance transformation ratio and resonant frequency, and Q is found.

$R_P \approx R_s Q^2 = R_s \left(\frac{1}{\omega R_s C} \right)^2 = \frac{L^2}{R_s C}$
 $R_P R_s \approx \frac{L^2}{C} = Z_0^2$

Q is approximately the square root of the transformation ratio is given by

$Q = \sqrt{\frac{R_P}{R_s}}$

As long as $Q > 3$ or 4 , the error will be under 10% and $Q > 10$, the max error will be 1% or 50%.

THE PI-MATCH

Limitation of L match is we can specify two of center frequency, impedance transformation ratio and Q. To acquire third degree of freedom, the Pi-match and called because of its shade. Here the load resistance R_P is transformed to a lower resistance known as image or intermediate resistance.

IMPEDENCE MATCHING NETWORKS

Impedance Z is a measure of opposition to electrical flow. It is measured in Ohms.

For DC system, the impedance and resistance are same.

In AC system, the reactance enters the equation due to frequency dependent capacitor and inductor.


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

↓ Resistance

+ inductive reactance

- capacitive reactance

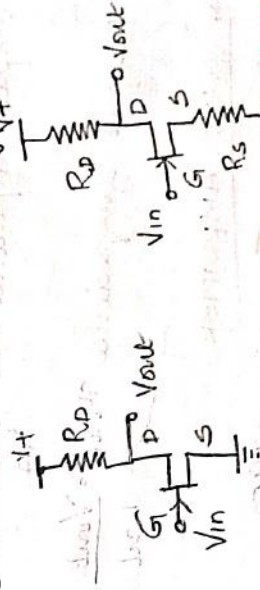
Impedance matching is designing source and load impedance to minimize signal reflection or maximize power transfer. In DC, the source and load should be equal. In AC, the source should either be equal to the load or complex conjugate of the load.



AMPLIFIERS: COMMON SOURCE, COMMON GATE

- In common source configuration, the FET exhibits high input impedance, high gain, potential instability and low noise figure.
- * High source and load impedance are required by the device for high gain.

 THE T-MATCH
In this single capacitor implementation, the is decomposed into two equal one. The Parallel (image) reactance is seen across the capacitor.



The net Q is

$$Q = \omega_0 R_{in} (C_1 + C_2)$$

image reactance

$$= \sqrt{\frac{R_{in}}{R_{th}} - 1} + \sqrt{\frac{R_{th}}{R_L} - 1}$$

From which image reactance

$$C_1 + C_2 = \frac{Q}{\omega_0 R_{in}}$$

$$L_1 = \frac{Q \sqrt{R_{in} R_{th}}}{\omega_0}$$

$$L_2 = \frac{Q \sqrt{R_{th} R_L}}{\omega_0}$$

T match is particularly useful when source and termination parasitic are inductive nature.

This amplifier can work as either
 * transconductance amplifier
 * voltage amplifier.

If amplifier works as transconductance
 then, the input signals are amplified and
 modulated the current flowing to the
 load.

If amplifier working as voltage amplifier
 the input signal is amplified and
 modulates the current passing through
 the FET and changes the voltage across
 the load resistor according to Ohm's law

Current gain $A_i = \frac{i_{out}}{i_{in}}$

Voltage gain $A_V = \frac{V_{out}}{V_{in}}$


Input impedance $Z_{in} = \frac{V_{in}}{i_{in}}$

Output impedance $Z_{out} = \frac{V_{out}}{i_{out}}$

COMMON GATE AMPLIFIER

In common gate configuration.

 The FET generally exhibits high gain, high
 output impedance, low input impedance
 unconditional stability and noise
 performance comparable to that of the
 common source mode.



This configuration is used less often than
 the common source or common follower.
 However, it can be combined with common
 source amplifiers to create cascode configuration.
 It is used in CMOS RF receivers when operating
 near the frequency limitations of FETs due to
 desirable impedance matching and potentially
 has lower noise.

short circuit current gain $A_i = \frac{i_{out}}{i_s} \Big|_{R_L=0}$


open circuit voltage gain $A_V = \frac{V_{out}}{V_s} \Big|_{R_L=0}$

Input resistance $R_{in} = \frac{V_s}{i_s}$

output resistance $R_{out} = \frac{V_x}{i_x}$

A common-gate amplifier is one of three
 basic single stage field-effect transistor (FET)
 amplifiers or current buffer or voltage amplifier

 * Capacitance between drain and gate transistor complicates calculation effort further




- * Mid Band gain can be calculated by assuming purely resistive impedance
- * Large valued capacitor used for AC coupling will be shorts in this analysis
- * For DC coupled circuits, typically DC gain = Mid gain
- * Small valued capacitor will be open in this analysis
- * we are interested in knowing the bandwidth
- Bandwidth is primarily set by the lowest frequency pole ω_0
- * Additional attenuation occurs at frequencies beyond the amplifier bandwidth by higher frequency poles ω_1, ω_2 etc
- * Open circuit time constant (OCT) technique allows to estimate bandwidth of amplifier circuit

The common source and common drain configurations have high input resistance because the gate is the input terminal. In common gate, the source is input terminal has low input resistance. Common Gate FET configuration provides low input impedance with high voltage gain, current gain is low and mid all power gain is low. Common gate amplifiers, often used in high frequency application and has much larger bandwidth.

Common gate amplifiers provides a power gain for the signal amplifier. The common gate Amplifier is used less often than the common source or source follower.

 DC TIME CONSTANT IN BANDWIDTH ESTIMATION AND ENHANCEMENT:



Two port analysis allows us to quickly calculate small signal gain from cascaded network stages when complex impedances are considered (ie: resistor, inductor and capacitor). * complex impedance calculations are time consuming.


HIGH FREQUENCY AMPLIFIER DESIGN.

* The design of amplifiers at high frequency demands more effort in reaching the performance when approaching the inherent limitations of the device

* The effect of parasitic capacitances and inductances can impose serious constraints on performance
 * A collection of useful bandwidth extension techniques shall be introduced.

The Shunt Peaked Amplifier.

 A standard common source amplifier with addition of inductor provides bandwidth enhancement.



Qualitative analysis.
 - frequency domain: introducing a 'zero'
 - time domain: step response.

This means that ω_1, ω_2 and higher poles are not close in frequency to ω_0 .
 let us assume the transfer function from V_{in} to V_{out}

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{K}{(T_0s + 1)(T_1s + 1) \dots (T_{n-1}s + 1)}$$

we are ignoring any ac coupling poles and zeros.
 which means DC gain = Midband gain.
 which is required to simplify the analysis.


DC gain equals k in as $s=0$
 The OCT approximates the transfer function as

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{K}{\left(\sum_{i=0}^{n-1} T_i\right) s + 1}$$

The estimated bandwidth is found by substituting $s = j\omega_0$ and solving for ω_0 such that magnitude is $1/\sqrt{2}$.

$$\omega_0 = \frac{1}{\sum_{i=0}^{n-1} T_i} \Rightarrow \left| \frac{V_{out}(j\omega_0)}{V_{in}(j\omega_0)} \right| = \left| \frac{K}{j\omega_0 + 1} \right| = K/\sqrt{2}$$


Zeros as Bandwidth Enhancers

 

Pole zero doublet:

$$H(s) = \frac{\alpha Ts + 1}{Ts + 1}$$

Two port Bandwidth Enhancement

 

series peaking only without H.

- maximum $\omega_2 = \sqrt{2}\omega_1$, smaller than shunt peaking provided by complex poles.

$m \equiv R^2 C / L^2 = 0$
 $m = 3$: maximally flat group delay, $\omega_2 = 1.36\omega_1$

The impedance of RLC network
 $Z(s) = (sL + R) \parallel \frac{1}{sC} = R \frac{s(L/R) + 1}{s^2 LC + sRC + 1}$

$$|Z(j\omega)| = R \frac{(\omega L/R)^2 + 1}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

* $\omega L/R^2$ increases as ω increases.
 $(1 - \omega^2 LC)^2$ decreases as ω increases.

Design and procedure

Given R and C, determine L

Introducing $m = RC \parallel LR = RC/T$ where

$$T = L/R$$

$$Z(s) = \frac{R(Ts + 1)}{s^2 T^2 m + sTm + 1}$$

$$\frac{|Z(j\omega)|}{R} = \frac{(\omega T)^2 + 1}{(1 - \omega^2 T^2 m)^2 + (\omega T m)^2}$$

$\omega_1 = 1/R$, the uncomposited -3dB frequency

$$\frac{\omega_2}{\omega_1} = \sqrt{\left(-\frac{m^2}{2} + m + 1\right) + \sqrt{\left(-\frac{m^2}{2} + m + 1\right)^2 + m^2}}$$


To max bandwidth set $d\omega^2/dm = 0$.

$$m = \sqrt{2} \approx 1.41$$

$$\omega_{2,max} = 1.85\omega_1$$

m leads to 20% peak in frequency

The Shunt Series Amplifier

 

Effective gain g_m or G_m

$$G_m = i_d = \frac{g_m}{1 + g_m R_e}$$

$$\approx \frac{1}{R_e} \text{ if } R_e \gg 1/g_m$$

Assume R_f large enough, the voltage gain

$$A_v = -R_L/R_e$$

R_f reduces both input and output resistance through shunt feedback.

Input resistance R_{in}

$$R_{in} = \frac{R_f}{1 - A_v} \approx \frac{R_f}{1 + R_L/R_e}$$

output resistance R_{out}

$$R_{out} = \frac{R_f + R_s}{1 + R_s/R_e} \approx \frac{R_f}{1 + R_s/R_e}$$

if $R_L = R_s = R$

$$R_{in} \approx R_{out} \approx \frac{R_f}{1 + R/R_e} \approx \frac{R_f}{1 - A_v}$$

Gate to drain gain

$$V_{out} = -g_m \left(\frac{R_f R_L}{R_f + R_L} + V_{test} \frac{R_L}{R_f + R_L} \right)$$

$$A_v = \frac{V_{out}}{V_{test}} = -\frac{R_L}{R_e} \left[\frac{1}{1 + 1/g_m R_e} \right] \cdot \left[\frac{1}{1 + R_L/R_f} \right] \cdot \left[1 - \frac{1}{g_m R_e} \right]$$

$$A_v = -\frac{R_L}{R_e} \left[\frac{R_f - R_e}{R_f + R_e} \right]$$


Input Resistance

$$R_{in} = \frac{R_f}{1 - A_v} = \frac{R_e (R_f + R_L)}{R_e + R_L}$$

output Resistance

$$R_{out} = \frac{R_e (R_f + R_s)}{R_e + R_s}$$

Tuned Amplifier

 

- Drawing from a zero impedance source with neglect the series gate resistance. Then, C_{gd} can be absorbed into C.

The components in the responsive current

- * Resistive
- * Capacitive

Admittance seen to the right of C_{gs}

$$y_{in} = \frac{y_F + y_F}{y_F + y_F} + \frac{g_m y_F}{y_F + y_F}$$

where $y_F = j\omega C_{gd}$ and y_F is the admittance of RLC tank

$$y_{in} \approx y_F + g_m (j\omega C_{gd}) y_F$$

- * y_F has a net negative imaginary part at frequency where the tank looks inductive
- * 2nd term on RHS of the above equation can have a negative resistance were connected to it.

* All are caused by the presence of C_{gd} which may be as much as 30-50% of main gate capacitance

Neutralization and unilateralization

Neutralization: Cannot be done precisely for C_{gd} is voltage-dependent.


The circuit is thus an ideal transistor driving an RLC tank

- * At the resonant frequency, the gain is $g_m R$.
- * The total -3dB bandwidth is $1/RC$
- * The product of gain and bandwidth is $\frac{g_m}{RC}$.

$$G.BW = g_m R \cdot \frac{1}{RC} = \frac{g_m}{C}$$

which is independent of center frequency.

 - * The key is the cancellation of the load capacitance by the inductor in tuned Amplifier



Admittance seen to the left of RLC tank (y_{out})

The result is a parallel $R_{eq} C_{eq}$

$$R_{eq} = R_s + r_g$$

$$C_{eq} = C_{gd} [1 + g_m R_{eq}]$$

$$= C_{gd} [1 + g_m (R_s + r_g)]$$

This is the alternative manifest of Miller Viewed from output port.

Maximize the overall BW

* Bandwidth Shrinkage

Assumption: Each stage has a unit DC gain and a single pole.

$$H(s) = \frac{1}{s+1}$$

A cascade of n such amplifiers

$$A(s) = \left(\frac{1}{(s+1)} \right)^n$$

$$|A(j\omega)| = \left| \frac{1}{j\omega T + 1} \right|^n = \frac{1}{\sqrt{2}}$$

so that

$$\left(\frac{1}{\sqrt{(T\omega)^2 + 1}} \right)^n = \frac{1}{\sqrt{2}}$$

The bandwidth is

$$\omega = \frac{1}{T} \sqrt{2^{1/n} - 1}$$

As n approaches infinity, the overall bandwidth tends towards zero to make


Physics make clear

$$2^{1/n} = \exp[\ln(2^{1/n})] = \exp\left(\frac{1}{n} \ln 2\right)$$


for large n ,

$$\exp\left(\frac{1}{n} \ln 2\right) \approx 1 + \frac{1}{n} \ln 2$$

 Thus $\omega = \frac{1}{T} \sqrt{2^{1/n} - 1} \approx \frac{1}{T} \sqrt{\frac{1}{n} \ln 2} \approx \frac{0.833}{T \sqrt{n}}$



 inductance and source-coupled version of cascode amplifier trade off for given total current and headroom



CASCODE AMPLIFIER.

- * How many amplifiers stages to use to achieve a certain gain?
- * Given a BW for each stage, what is BW of overall amplifier.
- * Any optimum number of stages to

which yields.

$$\ln(G^n) = \frac{1}{2} \Rightarrow G^{1/n} = e^{1/2} = 1.619$$

The number of stages corresponding to this optimum is

$$n = 2 \ln G$$

The overall bandwidth in this case is

$$BW_{tot} = W_1 \sqrt{\frac{\ln 2}{2 \ln G}} \approx \frac{0.357}{\sqrt{\ln G}} WT$$

It can be seen when n is chosen optimally (knowing G), the product of the bandwidth and the square root of the log of the gain is a constant. The overall bandwidth is relatively insensitive to the value of overall gain.

- * A Voltage step applied to input.
- * The input propagates down the input line causing a step to appear at each transistor in succession.
- * Each transistor generates a current ($gm \cdot v_{step}$)
- * ultimately all the transistor output currents are summed in time coherence

over all gain $AV = \frac{gm Z_o}{g}$

The error for $n=1$ is 17% and 28%. The drops pretty fast as n increases. The open circuit time constant method would predict the bandwidth goes directly as $1/n$, while in fact it goes as the reciprocal square root.

* optimum gain per stage. Assuming each stage is identical and width constant gain-bandwidth product. The goal is to find the number of stages that, for given overall gain requirement, maximizing the bandwidth.

over all gain G , meaning $G_{ss} = G^{1/n}$
Gain-bandwidth product for each stage: WT

$$BW_{ss} = \frac{WT}{G^{1/n}}$$

The bandwidth for the total Amplifier

$$BW_{tot} \approx \frac{WT \sqrt{\ln 2}}{G^{1/n} \sqrt{n}}$$

or $\frac{1}{BW_{tot}} \approx \frac{1}{WT \sqrt{\ln 2}} (\sqrt{n} G^{1/n})$.

The maximum total bandwidth is achieved when

$$\frac{d}{dn} (\sqrt{n} G^{1/n}) = 0$$

To develop design strategy that balances gain, input impedance, noise figure, power consumption, we will derive analytical expression for noise parameters directly from the device noise model.

Derivation of intrinsic mosfet Two port noise parameters

MOSFET noise model consist of two sources.

(i) mean square drain current noise

$$i_{nd}^2 = 4kT \gamma g_{do} \Delta f$$

(ii) gate current noise

$$i_{ng}^2 = 4kT \gamma g_{gg} \Delta f$$

$$\gamma g = \frac{w^2 c^2 g_s}{5g_{do}}$$

further gate noise is correlated with drain noise by correlation coefficient

$$C = \frac{\overline{i_{ng} i_{nd}}}{\sqrt{i_{ng}^2 i_{nd}^2}}$$

where reference direction for gate noise is from source to gate. drain noise is from drain to source

This amplifier has overall gain that depends linearly on the number of stages. Thus each stage can operate at frequencies where the gain is smaller than unity.

- can operate at substantially higher frequencies than conventional amplifier
- since delay is proportional to the number of stages, it trades gain for delay, not bandwidth.
- Transistor input/output capacitances are absorbed by delay line.
- Each stage can have gain smaller than unity, hence higher BW.
- Power hungry.

Low Noise Amplifier

The first stage of receiver is typically a LNA, whose main function is to provide enough gain to overcome the noise of subsequent stages (Mixers).

In principle, one can obtain minimum noise figure from a given device using optimum source impedance defined by 4 noise parameters G_o, B_o, R_o and G_{in} . This classical method faces power consumption.

under open circuit condition

dividing drain current noise by transconductance yields an equivalent input voltage, which when multiplied by input admittance yield equivalent input current noise and modeling of ind:

$$\overline{i_{ni}^2} = \overline{i_{nd}^2} (j\omega C_{gs})^2 = \frac{4kT \gamma g_{do} \Delta f (j\omega C_{gs})^2}{g_m^2}$$

$$= e_n^2 (j\omega C_{gs})^2$$

we have assumed that input admittance of MOSFET is purely capacitive which is good for frequency below ω_T

The total equivalent input current noise is the sum of reflected drain noise and the induced gate current noise.

The induced gate noise current of a tone (i) $i_{ngc} \rightarrow$ fully correlated with drain current noise

(ii) $i_{ngu} \rightarrow$ uncorrelated with drain current noise.

The correlation admittance is

$$\gamma_c = \frac{i_{ngc}}{i_{nd}} = \frac{j\omega C_{gs} + i_{ngc}}{e_n} = \frac{j\omega C_{gs} + g_m \cdot i_{ngc}}{i_{nd}}$$

(3)

In long channel the value of γ_c (theoretically 0.395).

Assumptions

- * γ_c is constant at its long channel value and thermal noise due to channel gate material will be neglected

- * C_{gd} also be neglected to derive the equivalent 2-port noise parameters

$$R_n \equiv \frac{e_n^2}{4kT\Delta f}$$

$$G_u \equiv \frac{i_{nu}^2}{4kT\Delta f}$$

$$\gamma_c = \frac{i_c}{i_{nd}} = G_c + jB_c$$

To find input noise voltage

$$\overline{e_n^2} = \overline{i_{nd}^2} \frac{g_m^2}{4kT\gamma_{gd} \Delta f}$$

This input noise voltage is correlated and in phase with drain current noise.

$$R_n \equiv \frac{e_n^2}{4kT\Delta f} = \frac{\gamma_{gd}^2}{4kT\Delta f} g_m^2$$

To express Y_c in more useful form.
 we express in terms of cross-correlation
 by multiplying both numerator and
 denominator by conjugate of drain noise
 current.

$$\begin{aligned} \frac{g_m \cdot \text{In}g_c}{i_{nd}} &= \frac{g_m \cdot \text{In}g_c \cdot i_{nd}^*}{i_{nd} \cdot i_{nd}^*} \\ &= \frac{g_m \cdot \text{In}g_c \cdot i_{nd}^*}{i_{nd}^2} \\ &= \frac{g_m \cdot \text{In}g_c \cdot i_{nd}^*}{i_{nd}^2} \end{aligned}$$

The last equality
 In g is replaced by $i_{ng}c$

$$\begin{aligned} Y_c &= j\omega C g_s + g_m \cdot \frac{\text{In}g_c \cdot i_{nd}^*}{i_{nd}^2} \\ &= j\omega C g_s + g_m \cdot \frac{\text{In}g_c \cdot i_{nd}^*}{\sqrt{i_{ng}^2} \sqrt{i_{nd}^2}} \sqrt{\frac{i_{ng}}{i_{ng}}} \\ Y_c &= j\omega C g_s + g_m \cdot \frac{\text{In}g_c \cdot i_{nd}^*}{\sqrt{i_{ng} \cdot i_{nd}^2}} \sqrt{\frac{i_{ng}}{i_{nd}^2}} \\ &= j\omega C g_s + g_m \cdot c \sqrt{\frac{i_{ng}}{i_{nd}^2}} \end{aligned}$$

Substitute for radical terms.

$$\begin{aligned} Y_c &= j\omega C g_s + g_m \cdot c \sqrt{\frac{\delta \omega^2 C g_s^2}{5 \cdot r g_{d0}^2}} \\ &= j\omega C g_s + \frac{g_m}{g_{d0}} \cdot c \sqrt{\frac{\delta}{5r}} \cdot \omega C g_s \end{aligned}$$

c is purely imaginary.

$$\begin{aligned} Y_c &= j\omega C g_s - j\omega C g_s \frac{g_m}{g_{d0}} \cdot |c| \sqrt{\frac{\delta}{5r}} \\ &= j\omega C g_s (1 - \alpha |c| \sqrt{\frac{\delta}{5r}}) \end{aligned}$$

where $\alpha = \frac{g_m}{g_{d0}}$ and unity for long
 channel devices.

Further noise

$$\begin{aligned} \text{In}g^2 &= (\text{In}g_c \text{In}g_u)^2 = 4kT \Delta f \delta g g |c|^2 + 4kT \Delta f \delta g g (1 - |c|^2) \\ &\quad \downarrow \\ &\quad \text{uncorrelated } g \text{ gate noise current} \end{aligned}$$

$$G_u \equiv \frac{i_u^2}{4kT \Delta f} = \frac{4kT \Delta f \delta g g (1 - |c|^2)}{4kT \Delta f} = \frac{\delta \omega^2 C g_s^2 (1 - |c|^2)}{5g_{d0}}$$


$$B_{opt} = -B_c = -\omega C g_s (1 - \alpha |c| \sqrt{\frac{\delta}{5r}})$$

(optimum source impedance)

The subscript 0 identifies the unit device of width W_0 . The noise factor F is a dimensionless quantity and therefore independent of width.

→ maximum gain
POWER MATCH VERSUS NOISE MATCH

 * The input impedance of MOSFET is inherently capacitive, so providing a good match to a 50Ω source without degrading noise performance would be difficult.



broadband 50Ω to put 50Ω resistor across the input terminal of common-source amplifier.
 Resistor R_1 adds thermal noise of own.
 The combination of these two effects produce high noise figure.

$$G_{opt} = \sqrt{\frac{G_{11}}{R_n} + G_c^2} = \alpha W C G_0 \sqrt{\frac{8}{5\gamma} (1 - |c|^2)}$$

(Optimum source admittance)

The minimum noise figure is given by.

$$F_{min} = 1 + 2R_n [G_{opt} + G_c] \approx 1 + \frac{2}{\sqrt{5}} \frac{W}{WT} \sqrt{\gamma 8 (1 - |c|^2)}$$

* If there is no gate current noise, the minimum noise figure would be 0 dB.

* The improvement in WT that accompany technology scaling improve noise figure at any given frequency.

The noise parameter for a device of width W are

$$G_c = \frac{W_0}{W} G_{c0}$$

$$B_c = \frac{W}{W_0} B_{c0}$$

$$G_0 = \frac{W}{W_0} G_{00}$$

$$R_n = \frac{W_0}{W} R_{n0}$$


This circuit is used in many applications even though its noise figure is not minimum possible.

Another method is for realizing a resistive input impedance is to use a common gate configuration. The resistance looking into source is $1/g_m$, a proper selection of device size and bias current can provide desired 50- Ω resistance.

With circuit it is straight to establish lower bound on noise figure of CG Amplifier.

$$F > 1 + r_n/\alpha$$

 All since topology suffer noise figure degradation from presence of noisy resistance in signal path, which is rectified by



impedance transformation model.

This amplifier is ideal except for frequency dependent of gain A(s). The input terminal is analogous to the gate terminal and amplifier is connected


$$F > 2 + \frac{r_n}{\alpha} \cdot \frac{1}{g_m R}$$

where $R_s = R_i = R$

This bound applies in low frequency limit and ignores gate current noise.

The shunt series amplifier.

 Provides a broad band real input impedance. Since it not reduce the signal with a noisy attenuator before amplifier as NF better that of circuit as



Disadvantages:

suffers from fewer problems yet resistive feedback generate thermal noise on its own and fails to present transmission impedance that equals Z_{opt} at all frequencies as a result, overall amplifier noise figure, usually of above circuit exceeds the device F_{min} by considerable amount.

to bottom plate of gate capacitance. The input impedance is

$$Z_{in} = \frac{1}{sC[1+A(s)]}$$

A(s) have gain and phase shift.

$$A(s) = A_0 e^{-j\phi}$$

then

$$Z_{in} = \frac{1}{j\omega C [1 + A_0 \cos\phi] + A_0 \omega C \sin\phi}$$

$$Y_{in} = j\omega C [1 + A_0 \cos\phi] + A_0 \omega C \sin\phi$$


* Phase lag grows with frequency and with square of frequency to a good approximation

* Transit time effects also cause a resistive component of input impedance.

* To enhance this effect we will create a resistive input impedance without noise of real resistors.

* A better method to employ inductive source degeneration [current lags behind gate voltage and advantage at control over real part of impedance]

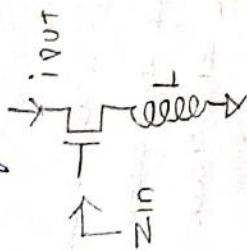of inductance from computing output resistance of circuit



For simple analysis a device model with transconductance and gate source capacitance is considered.

$$Z_{in} = sL + \frac{1}{sC_{gs}} + \frac{g_m}{sC_{gs}} L \approx sL + \frac{1}{sC_{gs}} + \frac{g_m L}{sC_{gs}}$$

The input impedance of RLC N/w with resistive term is \propto to inductive value

The source degeneration impedance Z_{is} modified by factor equal to $[B(y\omega) + 1]$.

$$\text{where } B(y\omega) = \frac{\omega T}{j\omega}$$

current gain magnitude goes to unity at ωT and capacitive phase angle due to C_{gs}

$$Z_{in}(j\omega) = \frac{1}{j\omega C_{gs}} + [B(y\omega) + 1]Z$$


$$= \frac{1}{j\omega C_{gs}} + Z + \left[\frac{\omega T}{j\omega} \right] Z$$

The capacitive degeneration causes negative resistance to the input impedance.

SINGLE ENDED AND DIFFERENTIAL LNA

SINGLE ENDED

 For narrowband applications it is advantageous to tune out the output capacitance to increase the gain.



- * Cascoding transistor M2 is used to reduce the interaction of tuned output with the tuned input and reduce the effect of M1's c_{gd} .
- * The total node capacitance at drain of M2 resonates with inductance L_d both to increase gain at center frequency and provide desired Band Pass filtering.

The input and output resonances are set equal to each other. If vary from each other flatter and broader response is obtained.

- * Transistor M3 is for a current mirror with M1 and its width is some small fractions of M1's width to minimize the power over head of bias circuit.
- * current through M3 is set by the supply voltage and R_{ref} in conjunction with V_{gs} of M3.
- * The resistor R_{BIAS} is chosen large so that more current is small and ignored.
- * To complete DC blocking, capacitor CB is to prevent upsetting the gate to source bias of M1. The value of CB is chosen to have a negligible reactance at signal frequency.
- To determine component value and device size.


Assuming

- (i) operation at 10 GHz, resistance - 50 Ω
 - (ii) 5-mA bias current for M1, for 0.5 μm technology. $L_{eff} = 0.35 \mu m$ and $C_{ox} = 3.8 \text{ mF/m}^2$
- from this we calculate
- (1) optimum width of main input M1 transistor $\approx 500 \mu m$ at bias current of 5mA, W/L is 35 Grps, $\mu = 0.95$

DIFFERENTIAL LNA

The disadvantage of single ended LNA is its sensitivity to parasitic ground inductance. The ground return of signal source is supposed to be at same potential as the inductor source of degenerating inductor, thus there is difference in these potentials because there is non-zero impedance between the two points.

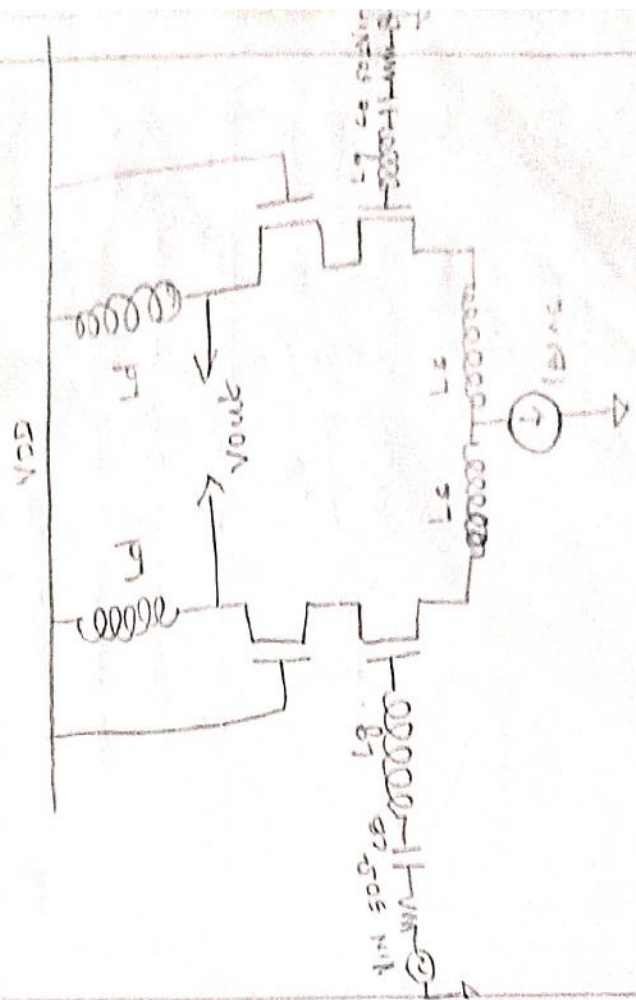Alternative method is to enclose ground located at symmetrical part of a differential structure any parasitic would rise in series with an impedance a still some constant



To find degeneration inductance to generate real part of 50 Ohms, LS must be 11.4nH

if Cgs must be known 20.5 pF. For resonating this capacitance at 10 GHz

The parasitic LNA, The bias inductor width and current are arbitrarily chosen as 1/10th of main transistor.

The resistive component is given by

$$Re[Zin] = \frac{wL^2 S}{1 + 2Cgd/Cgs}$$

The degenerating inductance must transfer be unbalanced to compensate.

The drain noise component whose

value is given by

$$Ind_{sub} = \frac{4kT R_{sub} g_{mb}^2 \Delta f}{1 + (w R_{sub} C_{gs})^2}$$

At frequencies below pole frequency of $w R_{sub} C_{gs}$, this extreme noise contribution remains negligible.

$$R_{sub} \leq 2R_s$$

* Another attribute, its ability to reject common mode disturbances

* The noise figure in this amplifier is higher than its single ended counterpart

* The power consumed is twice in single-ended amplifier to achieve the same noise figure and the disadvantage is the improved linearity that attends dividing the input voltage between two devices.

* The operational amplifier compares this voltage with the common-mode drain voltage of input pair and drives the gate of cascoding transistor to make the two voltages

$$V_{d1,2} = \frac{R_4}{R_3 + R_4} V_{gs1,2}$$

UNIT - III
 FEEDBACK SYSTEMS AND POWER AMPLIFIER

Feedback systems: Stability of feedback systems - Gain and phase margin, Root-locus
 Systems - Gain and frequency domain Techniques, Time and frequency domain Considerations, compensations, - Power Amplifier: General model - Class A, AB, B, C, D, E and F Amplifiers - Linearization Techniques - Efficiency boosting Techniques - ACPR metric.


FEEDBACK SYSTEMS:

History of modern feedback. * Application of feedback concepts is very ancient. * The first serious applications of feedback principles in electronic was by Rocket Pioneer Robert Goddard in 1912, a vacuum tube oscillator that employs positive feedback

ARMSTRONG AND ATAD THE REGENERATIVE

AMPLIFIERS:

 This paper on vacuum tube by Armstrong in 1915 explains how positive feedback (regeneration) could be used to greatly increase the voltage gain.



where a is forward gain, f is feedback gain, a , represents the gain of ordinary (open loop) f - represents the fraction of o/p voltage is fed back to the amplifier input

Overall gain of this amplifier

$$\sigma = V_{in} + f \cdot V_{out}$$

$$V_{out} = a \cdot \sigma = a (V_{in} + f \cdot V_{out})$$

Solving for input and output transfer function

$$A = \frac{a}{1 - af}$$

Any positive value of af , small than unity gives us an overall gain A , that exceeds a , the ordinary gain of vacuum tube amplifier. If $af = 0.9$, the overall gain is increased ten times of a .

If af is product of 0.99 where a is 100 fold time gain increases.

In this way, he was able to obtain gain from single stage, which other could obtain by cascading, which allowed the construction of relatively in expensive, high gain receivers and enabled reduction in transmitter power because of enhanced sensitivity provided by this increased gain.

HAROLD BLACK AND THE FEED FORWARD AMPLIFIER.


* Although Armstrong's regenerative amplifier solve the problem of obtaining large gain from vacuum tube amplifier, a different problem is telephone industry occupied when trying to extend long distance communication, the amplifier needed to compensate for transmission lines attenuation. Amplifiers around 1000-2000 those days could achieve around 1000-2000 miles but the quality was poor.

After long weeks, a crude transcontinental telephone service was found in 1915 by Alexander Graham Bell at 68 yrs. The problem was just not inefficient amplification, but was distortion. Each amplifier contributed 1% of distortion and in cascading that did not match the input.

* A small signal operation was opted but it was quite inefficient as it required the construction of milliwatt amplifiers for processing of milliwatt signals.

* And in 192, Harold Black found Bell laboratories, he became aware of this distortion and found restoring amplifier known as feed forward correction.

 The basic idea is to build 2 identical amplifiers and use one amplifier to subtract out the distortion of the first.



* There is no feedback and signals move forward only from input to output.
 * Z - time delay elements, which compensate for group delay of each amplifier, ensuring subtraction operation on signals that have experienced equal delays in travelling the over all system.

* Linear gain A, non linear gain \bar{A}
 * The input is given to amplifier and produces nominal gain A and produces some distortion in the process and its output is $A*V_{IN} + E$ → error voltage (where assumed to be small)

* The output of 1st amplifier is given to linear attenuator whose gain is $1/A$

The overall gain is

$$A = \frac{a}{1+af}$$

makeup product much larger than unity

Observations
 $A \approx 1/f$

- * The feedback factor f can be implemented with linear elements like resistive voltage divider, so that over all closed loop behaviour is linear even though, the amplifier in block a is not
- * closed loop gain A is much smaller than forward gain but, if gain is cheap but not distortion and best solution for is negative feedback.

DESENSITIVITY OF NEGATIVE FEEDBACK SYSTEMS.

There are some wild claims about negative feedback

- (i) It increases bandwidth
- (ii) It decreases distortion
- (iii) It reduces noise
- (iv) removes unsightly facial blemishes.

One absolute fundamental benefit is the desensitizing (ie) the overall passes an attenuator sensitivity to changes in the forward gain a

The attenuator output is subtracted from the input to get voltage which is perfectly scaled version of distortion.

* This pure distortion signal feeds to another amplifier. Because when have assumed distortion is small in first stage we expect and produces excellent linearity and produces excellent approximation to the original distortion


* The distortion from second amplifier is subtracted from the distorted signal of first amplifier to yield final output that has greatly reduced distortion.

Disadvantages

- Pinned impractical with old technology.
- It is virtually impossible to maintain tight level of matching to make feed forward amplifier more useful.

THE NEGATIVE FEEDBACK AMPLIFIER.

 
On August 1927, the idea of negative feedback amplifier came to him.



$$\frac{A}{f} \left(\frac{-af}{1+af} \right)$$

 (i) Negative feedback extends bandwidth. The negative bandwidth is selectively throwing away gain at lower frequencies.

Let us suppose that forward gain is now a purely scalar quantity and is instead some $a(s)$ that rolls off with single pole behaviour, as long as af had magnitude large compared with unity, the closed loop gain equal to reciprocal of feedback gain magnitude.



Plotting $|a(s)|$ and $|1/f|$ on same graph.

- * If $|1/f|$ is much lower than $|a(s)| \rightarrow a(s)f$ has large magnitude and therefore closed loop behaviour is approximately $1/f$.
- * If $|1/f|$ is much higher than $|a(s)|$, $a(s)f$ has small magnitude and closed loop behaviour converges to $a(s)$.

if $af \gg 1$
 the quantity this notation of desensitization
 lets calculate differential change in A that
 result from differential change in a .

$$\frac{dA}{da} = \frac{d}{da} \left(\frac{a}{1+af} \right) = \frac{1}{(1+af)^2} = \frac{1}{a} \left(\frac{1}{1+af} \right)$$

By Re-arranging


$$\frac{dA}{A} = \frac{da}{a} \left(\frac{1}{1+af} \right)$$

The above equation tell us that given fractional change in A equals the fractional change in a , attenuated ("desensitized") by a factor of $1+af$. For this reason, the quantity $1+af$ is often called the desensitization of a feedback system.

* If forward gain varies with time, temperature, or i/p amplitude, the closed-loop gain exhibits smaller variations since they are attenuated by desensitization factor. If factor of is large, the desensitization will be large and variation in A due to change in a .

$$\frac{dA}{dA} = \frac{d}{dA} \left(\frac{a}{1+af} \right) = - \frac{a^2}{(1+af)^2}$$

 But gain to other noise sources are smaller which is a benefit.



To understand the idea that nothing happens with negative feedback just to have gain between two nodes, where noise signal would enter.

We choose K , for which the input and output transfer functions of the feedback and open loop amplifiers are same for every input. Thus feedback offers no noise reduction beyond what open-loop system could give.

Finally, the desensitizing to the forward gain is the only benefit conferred by negative feedback which is fundamental one.

STABILITY OF FEEDBACK SYSTEMS

The use of negative feedback allows the closed-loop transfer function $A(s)$ to approach the reciprocal of feedback gain f as (minus) the loop transmission $a(s)f(s)$ increases,

(ii) Negative feedback reduces noise.
 * Actually negative feedback cannot reduce input-referred noise of a system.
 * In most practical cases feedback typically increases the input-referred noise.


The idea that negative feedback reduces noise stems, for such systems the transfer functions are

$$\frac{V_{out}}{V_{in}} = \frac{a_1 a_2}{1 + a_1 a_2 f}$$

$$\frac{V_{out}}{V_{n1}} = \frac{a_1 a_2}{1 + a_1 a_2 f}$$


$$\frac{V_{out}}{V_{n2}} = \frac{a_2}{1 + a_1 a_2 f}$$
 
$$\frac{V_{out}}{V_{n3}} = \frac{1}{1 + a_1 a_2 f}$$



From these eqn, the gain from noise sources V_{n1} to the output is same as that the input to the output as amplifier cannot differentiate input and V_{n1} and enters the same point.

 We use BIBO definition of stability which states that a system is stable if every bounded input produces a bounded output. A system is BIBO stable if all poles of $H(s)$ are open left half plane.



To apply this test to our feedback system we must find poles of $A(s)$, the roots of $P(s) = 1 + a(s)f(s)$.

Determination of loop transmission is usually straight forward, whereas the closed loop transfer function requires identification of forward path and an additional mathematical step. Hence any method can determine stability from examination of loop transmission.

GAIN AND PHASE MARGIN AS STABILITY MEASURE

For stability consideration, to determine whether sine wave actually sine wave exist requires the use of nyquist stability test. which is complicated and many fail to use it.

Stability measure is used instead of nyquist test to find quantities like Phase margin and gain Margin.

(i) Gain Margin: Find frequency at which phase shift of $a(j\omega)f(j\omega)$ is -180° called ω_{180} . Then gain Margin

$$GM = \frac{1}{|a(j\omega_{180})f(j\omega_{180})|}$$

(ii) Phase Margin - The frequency at which magnitude of $a(j\omega)f(j\omega)$ is unity. call this frequency ω_c , the cross over frequency.

$$\text{Phase margin} = 180^\circ + \angle [a(j\omega_c)f(j\omega_c)]$$

ROOT LOCUS TECHNIQUE.

Gain and Phase use behaviour of loop transmission to determine the stability of closed loop system.

* To find roots of the polynomial $1 + a(s)f(s)$

$$P(s) = 1 + a(s)f(s) = 0$$

$$\Rightarrow a(s)f(s) = -1.$$

may decompose as magnitude and Phase angle for loop transmission.

is independent of k

$$C \cdot \prod_{j=1}^n (s + s_j) = C \cdot [s^n + s^{n-1} \sum_{j=1}^n s_j + \dots]$$

$$\prod_{j=1}^n s_j = L(s)$$

$$g(s) = p(s) / q(s)$$

$$p(s) = q(s) + k p(s)$$

Rule 4: As $k \rightarrow \infty$, $P \rightarrow z$ branches into ∞

$$Q_n = \frac{(2n+1) \cdot 180}{P-z}$$

Rule 5:

$$\sigma = \frac{\sum \text{Re}(\text{poles}) - \sum \text{Re}(\text{zeros})}{P-z}$$

$$p(s) = 1 + C_1 \cdot \frac{[s^2 + s^{-1} \sum_{i=1}^z \text{Re}(z_{\text{zeros}})]}{s^p + s^{p-1} \sum_{i=1}^p \text{Re}(p_{\text{poles}}) + \dots}$$

$$Q_n = 1 + C_1$$

$$s^{p-z} + s^{p-z-1} [\sum \text{Re}(\text{poles}) - \sum \text{Re}(z_{\text{zeros}})]$$

Rule 6: If real axis branch of locus lies b/w a pair of poles then locus breaks away from the real axis between the poles.

$$|a(s) f(s)| = 1$$

$$L[a(s) f(s)] = (2n+1) \cdot 180$$

Rule 1: The locus starts at the poles of the loop transmission and it terminates on the zeros of loop transmission.

Suppose $a(s) f(s)$ as $k g(s)$. $k \rightarrow$ gain factor and varying $g(s)$.

$$|g(s)| = \frac{1}{k}$$

where $g(s)$ must be large for small value of k . hence s satisfy magnitude, conditions near pole of $g(s)$, and when small undecaying values of s near zeros of $g(s)$.

Rule 2: If a root locus branch lies on the real axis, it resides to the left of an odd number of left half plane poles + zeros and to the right of an odd number of right half plane poles + zeros.

$$g(s) = \prod_{i=1}^z (z_i s + 1)$$

$$\prod_{k=1}^p (z_k s + 1)$$

Rule 3: If number of poles exceeds the number of zeros by two or more, then average distance of poles to the imaginary axis is

ZEROS OF A(S)

How poles of A(s) behave is given by root locus, given poles and zeros of G(s).

$$A(s) = \frac{a(s)}{(1+acs)fc(s)}$$

FREQUENCY AND TIME DOMAIN CHARACTERISTICS OF FIRST ORDER AND SECOND ORDER SYSTEM.

Formulas for first-order low pass system.

Assume transfer function is

$$H(s) = \frac{1}{s+1}$$

$$t_n = 2.2 \ln 9 \approx 2.2 \tau = 2.2 / \omega_n$$

$$P_0 = MP = 1$$

$$t_p = \infty$$

$$t_s / 2\% \approx 4\tau$$

$$\xi_1 = \tau$$

$$\omega_p = 0$$

Formulas for second order system

$$H(s) = \left[\frac{s^2}{\omega_n^2} + 2 \frac{\xi s}{\omega_n} + 1 \right]^{-1}$$

$$t_n \approx 2.2 \tau = \frac{2.2}{\omega_n}$$

Rule 7: The locus forms an initial stage angle θ_p , with respect to complex pole or angle θ_z .

$$\theta_p = 180^\circ - \sum \angle [poles] + \sum \angle [zeros]$$

$$\theta_z = 180^\circ + \sum \angle [poles] - \sum \angle [zeros]$$

$$- \theta_p + \sum \angle [zeros] - \sum \angle [poles]$$

$$\theta_z + \sum \angle [zeros] - \sum \angle [poles]$$

Rule 8: If a particular value of s is known to lie on locus.

$$K = \frac{1}{|G(s)|}$$

ROOT-LOCUS RULES FOR POSITIVE FEEDBACK SYSTEM.

$$\angle G(s) = n \cdot 360^\circ$$

rules developed for negative feedback in which $K > 0$

Therefore all occurrence of $(2n+1) \cdot 180^\circ$ should be replaced with $n \cdot 360^\circ$.

$$-L(s) = \frac{R_2}{R_1 + R_2} \cdot G(s) = 10^{-2} \cdot G(s)$$

$$= 10^5$$

$$(s+1)(10^{-3}s+1)$$

$$\omega_c \approx 10^4 \text{ rps.}$$

A new desired cross over frequency.

$$|L(j10^3)| = 10^5$$

$$= \frac{10^5}{\sqrt{10^6 + 1} \cdot \sqrt{1 + 10^6}} \approx 70.7$$


old loop transmission

$$-L(s) = \frac{R_2}{R_1 + R_2} \cdot G(s) = \left(\frac{R_1}{R_2} + 1 \right)^{-1} = G(s)$$

New loop transmission

$$= L(s) = \left(\frac{R_1}{R_2 + 1} + 1 \right)^{-1} \cdot G(s)$$

$$R_2 = \frac{R_2}{70.4}$$

 

$$P_o = 1 + \exp\left(\frac{-\pi \xi}{\sqrt{1-\xi^2}}\right)$$

$$\zeta_p = \frac{T_{osc}}{2} = \frac{\pi}{\omega_n \sqrt{1-\xi^2}}$$

$$t_s|_{2\%} \approx 4T_{env} = \frac{4}{\xi \omega_n}$$

$$\xi_1 = \frac{2 \xi}{\omega_n}$$

$$\xi_p = \frac{1}{2 \xi \sqrt{1-\xi^2}}, \quad \xi < \frac{1}{\sqrt{2}}$$

$$\omega_p = \omega_n \sqrt{1-2\xi^2}, \quad \xi < \frac{1}{\sqrt{2}}$$

$$\omega_h = \omega_n \left[1 - 2\xi^2 + \sqrt{2-4\xi^2+4\xi^4} \right]^{1/2}$$

$$= \omega_n \xi = 1/\sqrt{2}$$

COMPENSATIONS

Compensations through Gain Reduction

$$\text{Example } G(s) = \frac{10^7}{(s+1)(10^{-3}s+1)}$$



LEAD COMPENSATION

We have seen phase margin can be improved by reducing the magnitude of loop transmission in order to lower the cross frequency.

An Alternative method to alter phase of loop transmission than its magnitude.

We wish to add positive or leading phase shift near cross over to improve phase margin.

Addition of capacitor gives us loop transmission to zero. As frequency increases, transmission through capacitor increases.

A zero provides an increase phase margin, magnitude addition to its positive phase shift.

$$-L(s) = \frac{R_2}{R_2 + [R_1 || 1/sC]} \cdot G(s)$$

which may be expressed as:

$$-L(s) = \left(\frac{R_2 + R_1}{R_1} \right) \left(\frac{sR_1C + 1}{sR_1C + 1 + R_1/R_2} \right) \cdot \frac{R_2}{R_2 + R_1} \cdot G(s)$$

LAG COMPENSATION

To decrease the real effect of compensator


$$-L(s) = \left[\frac{R_1}{R_2 || R + 1/sC} + 1 \right] \cdot G(s)$$

$$-L(s) = \frac{sRC + 1}{sC[R(1 + R_1/R_2) + R_1]} \cdot (1 + R_1/R_2) \cdot G(s)$$

$$-L(s) = \left\{ \frac{sRC + 1}{sC[R + R_1 || R_2] + 1} \right\} \cdot \frac{R_2}{R_1 + R_2} \cdot G(s)$$

At DC, the compensator transfer function is unity

$$C(s) \rightarrow \frac{R_1}{R_2 + (R_1 || R_2)}$$

 


FILTER, OSCILLATOR AND MIXER


Overview - basic resonator and filter configuration
 special filter realization, filter implementation
 Basic oscillator model, high frequency oscillator
 configuration, colpitt's configuration - basic
 characteristics of mixers, single and double
 balanced mixers.

BASIC RESONATOR AND FILTER CONFIGURATION


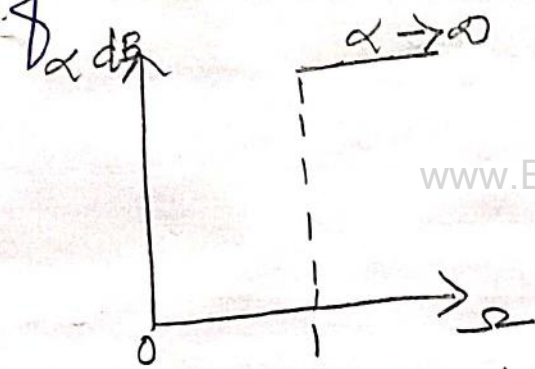
The ideal behaviour of four types of filters



Low pass filter

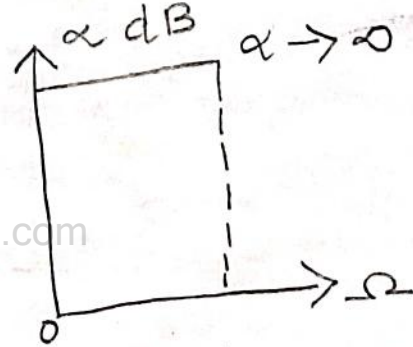



High pass filter

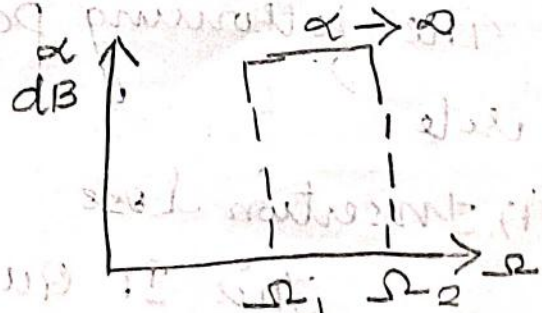 

$\Omega = \omega/\omega_c$ as normalized frequency.
 $\omega_c \rightarrow$ cut off frequency for low pass and high frequency.
 \rightarrow centre frequency for band pass and Band stop filter.

There are 3 standard filter approaches they are:

  - (i) binomial (Butterworth)
- (ii) chebyshev
- (iii) elliptic (Cauer) low pass filter.



The following parameters play a vital role:

- (i) Insertion Loss: This IL quantifies how much level the 0 dB line the power amplitude response drops.

$$IL = 10 \log \frac{P_{in}}{P_t} = -10 \log (1 - |T_{in}|^2)$$
- P_{in} \rightarrow Power input from source
- P_t \rightarrow Power delivered to load
- $|T_{in}|$ \rightarrow reflection coefficient

RIPPLE: The flatness of signal in passband can be quantified specifying the ripple or difference between maximum and minimum amplitude response in either dB or nepers.

BANDWIDTH: Bandwidth defines the difference between upper and lower frequencies typically recorded at 3dB attenuation point above passband $BW_{3dB} = f_u - f_l$


SHAPE FACTOR: This factor describes the sharpness of the filter by taking ratio between the 60dB and dB bandwidth $SF = \frac{BW_{60dB}}{BW_{3dB}} = \frac{f_u - f_l}{f_u^{3dB} - f_l^{3dB}}$

REJECTION: For ideal filter, the infinite attenuation level for undesirable signal frequencies. One additional parameter describes the sensitivity of filter is Q factor

$$Q = \frac{\text{average stored energy}}{\text{energy loss per cycle}} \quad W = \omega C$$

$$= \frac{\omega \text{ average stored energy}}{\omega - \omega_c} \quad \text{Power Loss} \quad \omega = \omega_c$$

 For any filter design, we to find V_2 due to V_1 input voltage V_1 or the generator voltage V_G .



The overall ABCD network is

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & R G \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/R_L & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+(R+R_G)(\delta\omega C + \frac{1}{R_L}) & R_G + R_L \\ \delta\omega C + \frac{1}{R_L} & 1 \end{bmatrix}$$

Both source impedance and load impedance are resistive (ie) $Z_G = R_G$ and $Z_L = R_L$.


$$\frac{V_2}{V_G} = \frac{1}{A} = \frac{1}{1+(R+R_G)(\delta\omega C + \frac{1}{R_L})}$$

$$\frac{V_2}{V_G} = \frac{1}{1+(R+R_G) \left(\frac{R_L}{R_G + R_L} \right)}$$

for $\omega \rightarrow \infty$, $\frac{V_2}{V_G} = 0$

Sn first order.
 
$$\frac{V_2}{V_G} = H(\omega) = \frac{1}{1+j\omega(R_G+R)L}$$






The power loss as consisting of power loss associated with external circuit and filter. The resulting Q factor is called loaded Q or Q_{LD} .

$$\frac{1}{Q_{LD}} = \frac{1}{\omega} \left[\frac{\text{Power loss in filter}}{\text{average stored energy}} \right]_{\omega=\omega_n} + \frac{1}{\omega} \left[\frac{\text{Power loss in load}}{\text{average stored energy}} \right]_{\omega=\omega_n}$$

$$\frac{1}{Q_{LD}} = \frac{1}{Q_F} + \frac{1}{Q_E} \text{ (filter) (external)}$$
  
$$Q_{LD} = \frac{fc}{f_u} \frac{3dB}{3dB - ft} = \frac{fc}{BW} \frac{3dB}{3dB}$$



 

$$\frac{V_2}{V_G} = \frac{I}{A} = \frac{1}{1+(R+RG)} \left[\frac{1}{j\omega L} + \frac{1}{R_L} \right]$$

as $\omega \rightarrow 0$

$$\frac{V_2}{V_G} = 0$$

as $\omega \rightarrow \infty$

$$\frac{V_2}{V_G} = \frac{1}{1+(R+RG)/R_L} = \frac{R_L}{R_G+R+R_L}$$

BANDPASS AND BANDSTOP FILTER

A Bandpass filter can be constructed through RLC series or through parallel connection of RLC shunt circuit.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_G \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/Z_L & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Z+Z_G}{Z_L} & Z_G+Z \\ \frac{1}{Z_L} & 1 \end{bmatrix}$$

$$\alpha(\omega) = -10 |H(\omega)| = -\frac{1}{20} \ln |H(\omega)|^2$$


$$\alpha(\omega) = -20 \log |H(\omega)| = -10 \log |H(\omega)|^2$$

Phase is


$$\phi(\omega) = \tan^{-1} \left[\frac{\text{Im}\{H(\omega)\}}{\text{Re}\{H(\omega)\}} \right]$$

Phase is called group delay by.

$$t_g = \frac{d\phi(\omega)}{d\omega}$$

 

(Attenuation profile)

 

(Phase response)

HIGH PASS FILTER

Replacing capacitor with inductor allows the construction of first order high pass filter.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & RG \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/j\omega L & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/R_L & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + (R+RG) & \frac{1}{j\omega L} + \frac{1}{R_L} \\ j\omega C + \frac{1}{R_L} & 1 \end{bmatrix}$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$H(\omega) = 1/A$$

$$\frac{V_2}{V_1} = H(\omega) = \frac{Z_L}{(Z_L + Z_G) + R + j\left[\omega L - \frac{1}{\omega C}\right]}$$

SPECIAL FILTER REALIZATIONS:

- There are 2 types of filters.
- (1) The maximally flat Butterworth.
- (2) The equi-ripple Chebyshev filter.

BUTTERWORTH-TYPE FILTER.

This filter type is known as maximally flat filter as its ripple is permitted in its attenuation profile.

$$|L| = -10 \log(1 - |T_{in}|^2) = 10 \log\{L.F.\}$$


$$= 10 \log[1 + a^2 \Omega^{2N}]$$

Ω - normalized frequency.

$N \rightarrow$ order of filter.


when $a=1$, $\Omega = \omega/\omega_c = 1$, then $L = 10 \log\{2\}$.

which is 3dB point at cut off frequency.

 

The elements are numbered 0 at generator side and g_{N+1} at load as elements alternate between series inductance and shunt capacitance!

 $g_0 =$ { internal generator resistance
 { internal generator conductance



$g_m =$ { inductance for series inductor
 { capacitance for shunt capacitor
 ($m=1, \dots, N$)

$g_{N+1} =$ { load reactance if last element is shunt capacitor
 { load conductance if last element is series inductor

Linear phase behaviour is more critical issue in wireless communication

$$\phi(\Omega) = A_1 \Omega - (1 + A_2 \Omega^{2N})$$

The associated group delay is

$$t_g = \frac{d\phi(\Omega)}{d\Omega} = A_1 [1 + A_2 (2N+1) \Omega^{2N}]$$

FILTER IMPLEMENTATION:

Filter design beyond 500 MHz are difficult to realize with discrete components because wavelength becomes comparable with physical wavelength resulting in loss that degrade the circuit performance. Thus to achieve at practical filters, the lumped to component filters must be converted to distributed element realization.

The necessary tools are

- (i) Richards Transformation
- (ii) the concept of unit element and
- (iii) Kuroda's identities.

These should a conversion be established between lumped and distributed design. Richard proposed a transformation that allows open- and short circuit transmission line segment to emulate inductive and capacitive behaviour of discrete components.

Impedance Z_{in} of short circuit line of characteristic line impedance Z_0 is reactive

$$Z_{in} = j Z_0 \tan(\beta l) = j Z_0 \tan \theta$$

reference frequency $f_0 = \frac{v_p}{\lambda_0}$

$$\theta = \beta Z_0 = \frac{2\pi f}{v_p} \frac{v_p}{8 f_0} = \frac{\pi f}{4 f_0} = \frac{\pi \Omega}{4}$$

$$j X_L = j \omega L = j Z_0 \tan \left[\frac{\pi}{4} \frac{f}{f_0} \right] = j Z_0 \tan \left[\frac{\pi \Omega}{4} \right] = S Z_0$$

CHEBYSHEV FILTER TYPE

The design of equal ripple filter type is described by chebyshev polynomial $T_N(\Omega)$

$$10 \log [LF] = 10 \log [1 + a^2 T_N^2(\Omega)]$$

$$T_N(\Omega) = \cos \{ N [\cos^{-1}(\Omega)] \}, \text{ for } |\Omega| \leq 1$$

$$T_N(\Omega) = \cosh \{ N [\cosh^{-1}(\Omega)] \}, \text{ for } |\Omega| > 1$$

The chebyshev polynomial in normalized frequency range $-1 < \Omega < 1$.


$$T_0 = 1, T_1 = \Omega, T_2 = -1 + 2\Omega^2, T_3 = -3\Omega + 4\Omega^3, T_4 = 1 - 8\Omega^2 + 8\Omega^4$$

$$|H(\Omega)| = \sqrt{H(\Omega)H(\Omega)^*} = \frac{1}{\sqrt{1 + a^2 T_N^2(\Omega)}}$$

with $a = 1, \Omega = 1$

we have

$$|H(0)| = \frac{1}{\sqrt{2}} = 0.707$$

 


where $S = j \tan(\frac{\pi \rho}{4})$ is actual Richards transform.
 $j B C = j \omega C = j Y_0 \tan(\frac{\pi \rho}{4}) = S Y_0$
 $Z_0 = 1$, and $Z_0 = 1/C$
 ρ/ρ_0 in length, a property that is known as commensurate line length.

UNIT ELEMENT:
 when converting lumped elements into transmission lines elements spatially to achieve practically realizable configuration by inserting so-called unit elements (UE's). The unit length has electric length of $\theta = \frac{\pi}{4} (f_1/f_0)$


$$[UE] = \begin{bmatrix} A_{UE} & B_{UE} \\ C_{UE} & D_{UE} \end{bmatrix} = \begin{bmatrix} \cos \theta & j Z_{UE} \sin \theta \\ \frac{j \sin \theta}{Z_{UE}} & \cos \theta \end{bmatrix} = \frac{1}{\sqrt{1-S^2}} \begin{bmatrix} 1 & Z_{UE} S \\ S & 1 \end{bmatrix}$$

KURODA'S IDENTITIES:
 It is important to convert a practically difficult-to-implement design to more suitable filter realization.

Initial Circuit

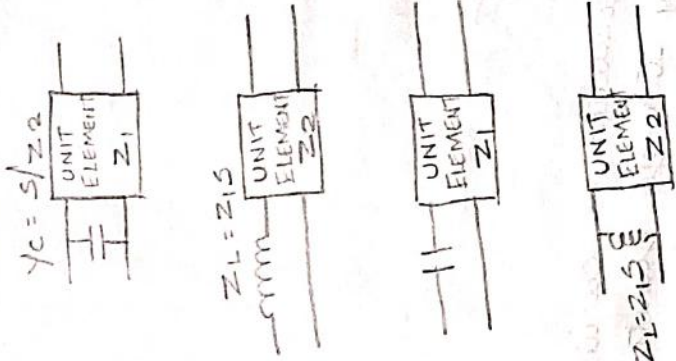

Kuroda's Identity

 


$$N = 1 + Z_2/Z_1$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_L = \begin{bmatrix} 1 & 0 \\ \frac{1}{SZ_1} & 1 \end{bmatrix} \frac{1}{\sqrt{1-S^2}} \begin{bmatrix} 1 & Z_2 S \\ S & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 S \\ \frac{S}{Z_2} & 1 \end{bmatrix}_{UE}$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_R = \frac{1}{\sqrt{1-S^2}} \begin{bmatrix} 1 & Z_2 S \\ \frac{SN}{Z_2} & 1 \end{bmatrix}_{UE} \begin{bmatrix} 1 & 0 \\ \frac{N}{SZ_1} & 1 \end{bmatrix}_{UE} \begin{bmatrix} 1 & 0 \\ 0 & N \end{bmatrix}_{trans}$$
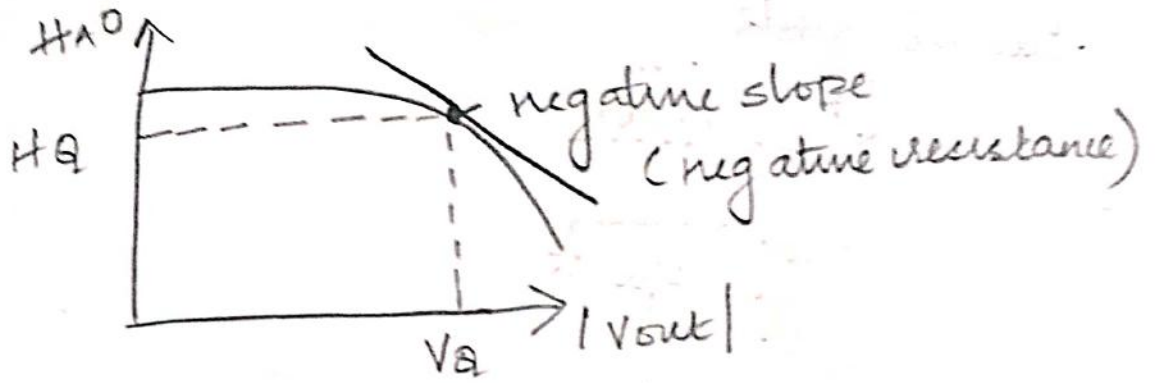
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_R = \frac{1}{\sqrt{1-S^2}} \begin{bmatrix} \frac{1}{N} (1 + \frac{Z_2}{Z_1}) & Z_2 S \\ \frac{S}{Z_2} + \frac{1}{SZ_1} & N \end{bmatrix}$$



Negative Resistance Oscillator.

is explained with RLC circuit.

 

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = -\frac{dV(t)}{dt}$$

$$i(t) = e^{\alpha t} (\hat{i}_1 e^{j\omega_0 t} + \hat{i}_2 e^{-j\omega_0 t})$$

where $\alpha = -R/2L$, $\omega_0 = \sqrt{1/(LC) - (R/2L)^2}$.

α is negative quantity


$$V(t) = V_0 + R_1 i + R_2 i^2 + \dots$$

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = \frac{dV(t)}{dt}$$


$$= -R_1 \frac{di(t)}{dt}$$

$$R + R_1 = 0$$

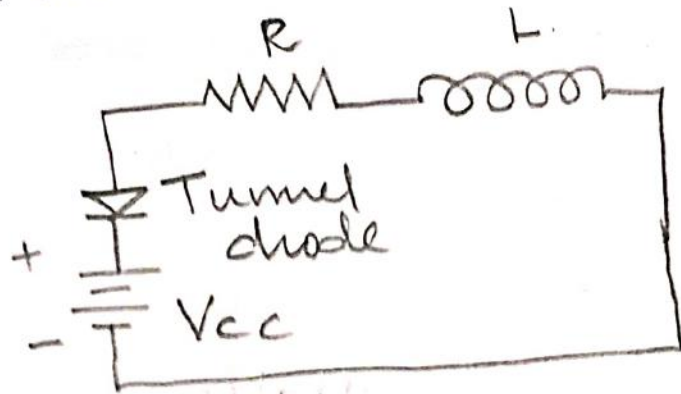
Negative resistance can be achieved by tunnel diode.



FEEDBACK OSCILLATOR DESIGN.

 

pi-type

 

T-type

$$H_F(w) = \frac{V_1}{V_{out}} = \frac{Z_1}{Z_1 + Z_3}$$

$$\mu_v V_1 + \hat{I}_B R_B + \hat{I}_B Z_C = 0$$

where $1/z_c = y_c = 1/z_2 + 1/(z_1 + z_3)$

$$H_A(\omega) = \frac{V_{out}}{V_i} = -\frac{\mu V}{Y_C R_B + 1}$$

closed transfer function is

$$H_T(\omega) H_A(\omega) = \frac{-\mu V Z_1 Z_2}{Z_2 Z_1 + Z_2 Z_3 + R_B(Z_1 + Z_2 + Z_3)}$$

$$\equiv 1.$$

$$X_3 = -(X_1 + X_2)$$

$$\frac{\mu V X_1 X_2}{-X_2 X_1 + X_2 (X_1 + X_2)} = \frac{\mu V}{X_2} X_1 = 1.$$

HIGH FREQUENCY OSCILLATOR CONFIGURATION

As operating frequency approaches GHz range the wave nature of voltage and current cannot be neglected.

The input reflection coefficient for matched source impedance

$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12} S_{21}}{1 - S_{22} \Gamma_L} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}$$

where $A = S_{11}S_{22} - S_{12}S_{21}$.

$$b_s = \sqrt{Z_0} / (Z_G + Z_0)$$

$$\frac{b_1}{b_s} = \frac{\Gamma_{in}}{1 - \Gamma_s \Gamma_{in}}$$

$$\Gamma_{in} \Gamma_s = 1$$

The identical circuits.

$$\Gamma_{out} \Gamma_L = 1$$

when stability factor $K = (1 - |S_{11}|^2 - |S_{22}|^2 + |A|^2) / (2|S_{12}||S_{21}|)$


$$K < 1$$


$$\Gamma_{in} \Gamma_s = 1$$

$$\Gamma_{out} \Gamma_L = 1$$

FIXED - FREQUENCY OSCILLATORS.
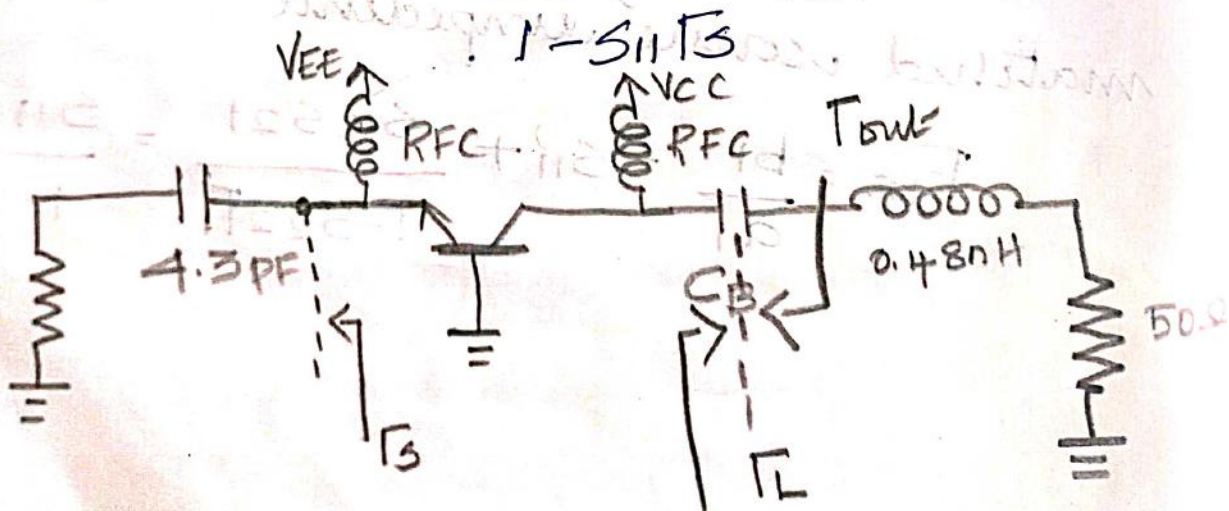
$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}}{1 - S_{11}\Gamma_s}$$



 

The unloaded Q or Q_u

$$Q_u = \frac{R}{\omega_0 L} = \omega_0 R C$$

the coupling coefficient β

$$\beta = \frac{R}{R_{ext}} = \frac{R}{2Z_0} = \frac{\omega_0 Q_u L}{2Z_0}$$

$$\omega_0 = 1/\sqrt{LC}$$


$$Q_u = \beta Q_E = (1 + \beta) Q_L$$

YIG - TUNED OSCILLATOR

The dielectric resonator allows tuning over a very narrow band, typically between 0.01 and 1%. such a tunable element, often of spherical shape called Yttrium iron garnet (YIG)

$$Q_u = -4\pi(Ms/3) + H_0$$

H_L

 

$$\omega_m = 2\pi \gamma (4\pi Ms) = 8\pi^2 \gamma Ms$$

γ - gyromagnetic ratio

$$\omega_0 = 2\pi \gamma H_0$$

$$L_0 = \frac{\mu_0 \omega_m}{\omega_0 d^2} \left[\frac{4}{3} \pi a^3 \right]$$

$$C_0 = L_0 \omega_0^2$$

Conductance


$$G_0 = \frac{d^2}{\mu_0 \omega_m Q_u \left[\frac{4}{3} \pi a^3 \right]}$$

COLPITTS OSCILLATOR

In colpitts oscillator realizations

$$X_1 = 1/\omega C_1, X_2 = 1/\omega C_2 \text{ and } X_3 = \omega L_3$$

 
where FET is active device. Here R_A , R_B and R_D and R_S set the DC bias point. C_S is RF by pass capacitor and C_B is blocking capacitor.



DESIGN STEPS:

The h-parameter configuration with the appropriate feedback loop is as shown.

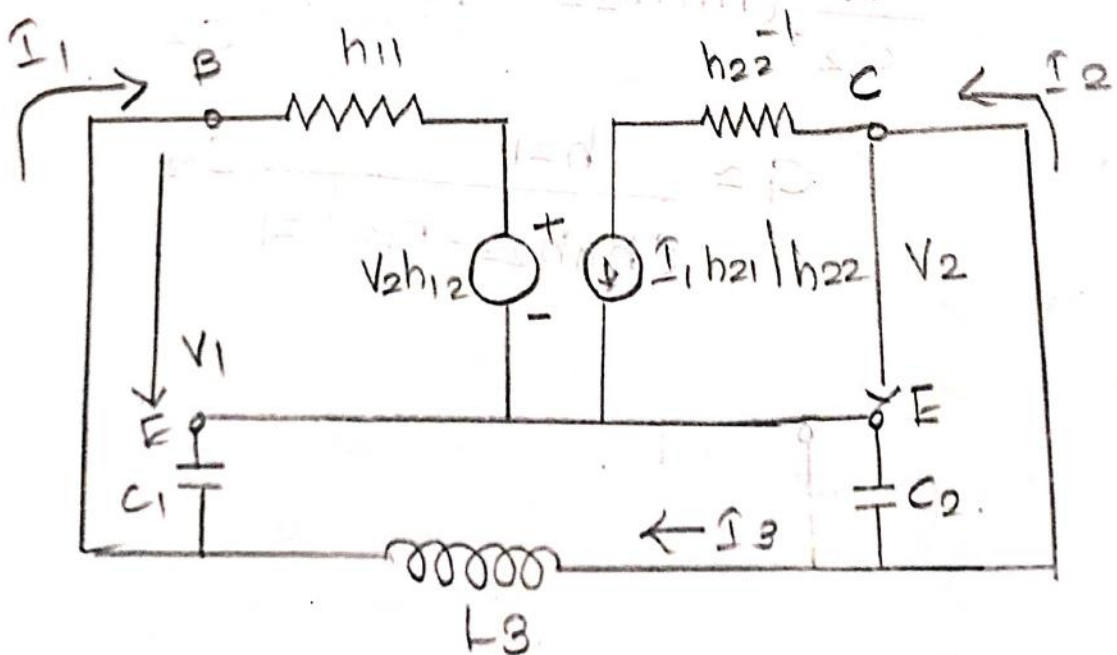The kirchoff voltage mesh equations involving input, output and feedback loops are given as $V_2 = V_{out} = I_2 h_{22}$



$$\left[h_{11} - j\omega C_1 \quad -\frac{h_{12}h_{21}}{h_{22}} \right] \frac{h_{12}}{h_{22}} \quad j\omega C_1$$

$$-\frac{h_{21}}{h_{22}} \quad \left(\frac{1}{h_{22}} - j\omega C_2 \right) \quad -j\omega C_2$$

$$j\omega C_1 \quad -j\omega C_2 \quad j(\omega L_3 - \omega C_1 - \omega C_2)$$


$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$f = \frac{1}{2\pi} \frac{1}{\sqrt{C_1 C_2}} \sqrt{h_{22}/h_{11} + (C_1 + C_2)/L_3}$$

$$\frac{C_1^2}{C_2^2} (h_{11}h_{22} - h_{12}h_{21}) - \frac{C_1}{C_2} h_{21} + 1 = 0$$

$$C_1 \approx \frac{h_{21}}{C_2 (h_{11}h_{22} - h_{12}h_{21})}$$

- * Mixers are commonly used to multiply signals of different frequencies.
- * A particular RF signal channel centered among many densely populated, narrowly spaced neighboring channels would require extremely high Q filters
- * The task becomes much manageable if RF signal carrier frequency can be reduced or downconverted within communication system. Perhaps one of the best known system is downconversion in a heterodyne receiver.

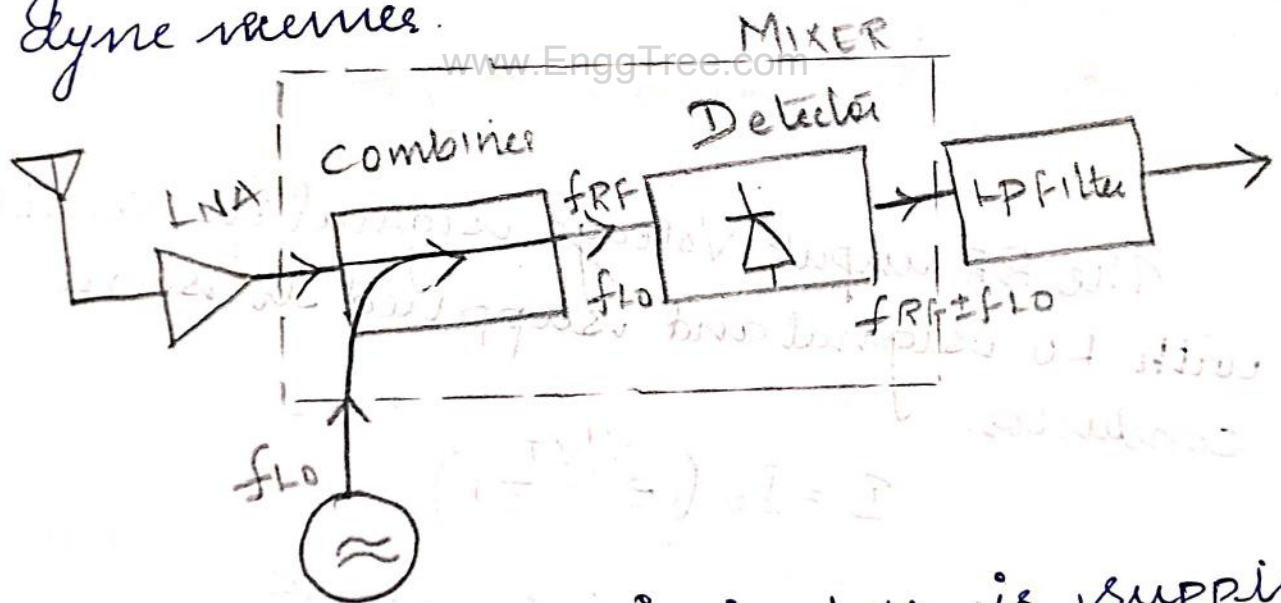


After preamplification in LNA, is supplied to a mixer whose task is to multiply the input signal of center frequency f_{RF} with with local oscillator (LO) frequency f_{LO} . The signal obtained after the mixer contains the frequencies $f_{RF} \pm f_{LO}$, of which after filtering, the lower

frequency component $f_{RF} = f_{LO}$ known as intermediate frequency IF.

The combiner and detector are constituting the mixer. The combiner is implemented through 90° or (180°) directional coupler.

 The mixer connected to an RF signal $V_{RF}(t)$ and local oscillator signal, $V_{LO}(t)$ known as pump signal.



The RF input voltage signal is combined with LO signal and supplied to semi-conductors.

$$I = I_0 (e^{V/V_T} - 1)$$

$$I(V) = I_{DSS} (1 - \sqrt{V/V_{TO}})^2$$

The input voltage is sum of RF signal $V_{RF} = V_{RF} \cos(\omega_{RF} t)$ and LO signal $V_{LO} = V_{LO} \cos(\omega_{LO} t)$ and bias V_Q .

$$V = V_Q + V_{RF} \cos(\omega_{RF} t) + V_{LO} \cos(\omega_{LO} t)$$

EnggTree.com

$$I(V) = I_0 + V \left[\frac{dI}{dV} \right]_{V_0} + \frac{1}{2} V^2 \left[\frac{d^2 I}{dV^2} \right]_{V_0} + \dots = I_0 + VA + V^2 B + \dots$$

$$I(V) = A \{ V_{RF} \cos(\omega_{RF} t) + V_{LO} \cos(\omega_{LO} t) + B \{ V_{RF}^2 \cos^2(\omega_{RF} t) + V_{LO}^2 \cos^2(\omega_{LO} t) \}$$

$$I(V) = \dots + BV_{RF} V_{LO} \{ \cos[(\omega_{RF} + \omega_{LO})t] + \cos[(\omega_{RF} - \omega_{LO})t] \}$$

which is Taylor series up to third term and this up to second order intermodular product ($V^2 \cdot B$).

Any higher order products such as third order intermodular product $V^3 C$ are neglected.


For diodes and BJTs these higher order harmonic term can significantly affect the performance of the mixer.

However second order intermodular product is the only surviving term if a FET with quadratic transfer characteristic is utilized.

SINGLE-BALANCED MIXER

The main disadvantage of these designs is the difficulty associated with providing LO energy while maintaining separation between LO, RF and RF signals for broadband applications.

 The balanced dual-diode or dual-transistor mixer in conjunction with hybrid coupler offers the ability to conduct such broad band operations and provides related noise suppression and spurious mode rejection. Spurs arise in oscillators and amplifiers due to parasitic resonance.




Balanced mixer employing a hybrid coupler

Besides an www.EnggTree.com WR, this design is capable of suppressing a considerable amount of noise because the opposite diode arrangement in conjunction with 90° phase shift provides a good degree of noise cancellation.

A more sophisticated design, with two MESFET and 90° and 180° hybrid coupler.

The 180° phase shift is needed since the second MESFET cannot be easily be reversed as done in anti-parallel diode configuration.

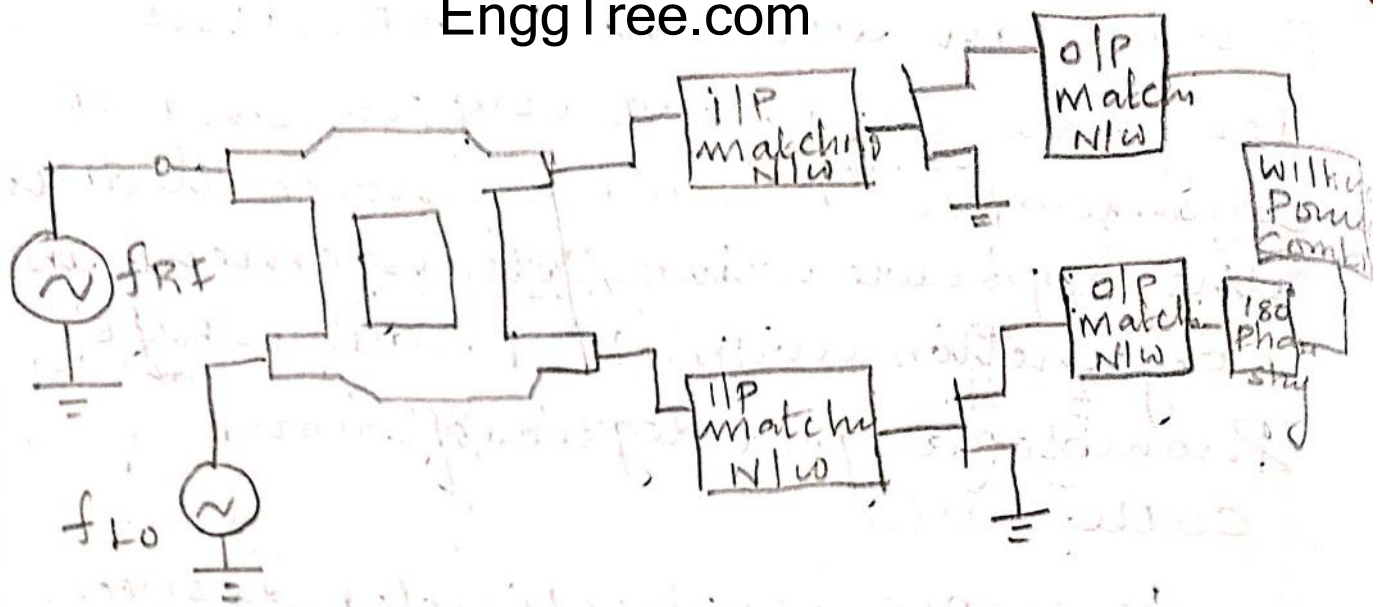It is also important to point out that this circuit exhibits LO to RF as well as LO to IF signal isolation, but no RF to IF signal isolation. For this reason, a low Pass filter is typically incorporated into output matching network of each of transistors.



DOUBLE-BALANCED MIXER

The double balanced mixer can be constructed by using four diodes arranged in rectified configuration.

The additional diodes provides better isolation and an improved suppression of spurious modes.


unlike the single balanced approach, the double balanced design eliminates all even harmonics of both the LO and RF signals.

The disadvantages are higher LO driver power and increased conversion loss.

All three signals path are decoupled and the input and output transformation enable a symmetric mixing with

SRIET/DEP.


me signal

 

PLL AND FREQUENCY SYNTHESIZERS

PLL: Linearized Model, Noise properties, Phase detectors, Loop filters and charge pumps - frequency synthesizers: Integer-N frequency synthesizers - Direct Digital frequency synthesizers


PLL: Linearized Model.

 

The basic PLL architecture consists of a phase detector and a Voltage Controlled Oscillator (VCO). The phase detector compares the phase of the incoming reference signal with that of VCO and produces an output that is some function of phase difference. The VCO simply generates a signal whose frequency is some function of control voltage.

The general idea is that the output of phase detector drives the VCO frequency in a direction that reduces the phase difference; that is the negative feedback system.

 once the loop achieves lock, the phase of input reference and VCO output signal ideally have fixed phase relationship



The linearized PLL model as above. Because we are generally interested in phase relation between the input and output variables, phase is the model.

Another consequence of choosing phase as input-output variable is that the VCO, whose output frequency depends on a control voltage, is modeled as an integrator, since phase is the integral of frequency. The VCO gain constant K_0 has units of radians per second per volt.

The phase detector is modeled as a simple subtractor that generates a phase error output ϕ_c that is the difference between the input and output phases. To accommodate gain scaling factors and the option of additional filtering in loop, a block with transfer function $H(s)$ is included.

FIRST-ORDER PLL

The simple PLL is one in which $H(s)$ is simply a scalar gain K_D with unit of Volt per radian. Because the loop transfer function possesses a single pole, this type of loop is known as first order PLL.

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{K_0 K_D}{s + K_0 K_D}$$

The closed loop bandwidth is

$$\omega_K = K_0 K_D$$

$$\frac{\phi_e(s)}{\phi_{in}(s)} = \frac{s}{s + K_0 K_D}$$

We assume input signal is a constant frequency sinusoid of frequency ω_i , then the phase ramps linearly with time at rate of ω_i radians per second.



By Laplace domain representation of input signal is

$$\phi_{in}(s) = \frac{\omega_i}{s^2}$$

$$\phi_e(s) = \frac{\omega_i}{s(s + K_0 K_D)}$$

By steady state error with constant frequency input is
  
$$\lim_{s \rightarrow 0} s \phi_c(s) = \frac{\omega_i}{K_0 K_D} = \frac{\omega_i}{\omega_b}$$



SECOND-ORDER PDK

In this model the constant K_D has units of volts per second because of extra integration.


As the loop transmission magnitude increases, the loop become progressively better damped because an increase in cross over frequency allows more of the zero's positive phase shift of negative phase shift of poles.

For very large loops transmissions, one closed loop pole end up at nearly the frequency of the zero, while the other

PLL AND FREQUENCY SYNTHESIZERS

PLL: Linearized Model, Noise properties, phase detectors, Loop filters and charge pumps - frequency synthesizers: Integer-N frequency synthesizers - Direct Digital frequency synthesizers


PLL: Linearized Model.

 

The basic PLL architecture consists of a phase detector and a Voltage Controlled Oscillator (VCO). The phase detector compares the phase of the incoming reference signal with that of VCO and produces an output that is some function of phase difference. The VCO simply generates a signal whose frequency is some function of control voltage.

The general idea is that the output of phase detector drives the VCO frequency in a direction that reduces the phase difference; that is the negative feedback system.

 once the loop achieves lock, the phase of input reference and VCO output signal ideally have fixed phase relationship.



The linearized PLL model as above, because we are generally interested in phase relation between the input and output variables are phase in this model.

Another consequence of choosing phase as input-output variable is that the VCO, whose output frequency depends on a control voltage, is modeled as an integrator, since phase is the integral of frequency. The VCO gain constant K_D has units of radians per second per volt.

The phase detector is modeled as a simple subtractor that generates a phase error output ϕ_c that is the difference between the input and output phases. To accommodate gain scaling factors and the option of additional filtering in loop, a block with transfer function $H'(s)$ is included.

FIRST-ORDER PLL

The simple PLL is one in which $H(s)$ is simply a scalar gain K_D with unit of Volt per radian. Because the loop transmission possesses a single pole, this type of loop is known as first order PLL.

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{K_0 K_D}{s + K_0 K_D}$$

The closed loop bandwidth is

$$\omega_K = K_0 K_D$$

$$\frac{\phi_e(s)}{\phi_{in}(s)} = \frac{s}{s + K_0 K_D}$$

We assume input signal is a constant frequency sinusoid of frequency ω_i , then the phase ramps linearly with time at rate of ω_i radians per second.



By Laplace domain representation of input signal is

$$\phi_{in}(s) = \frac{\omega_i}{s^2}$$

$$\phi_e(s) = \frac{\omega_i}{s(s + K_0 K_D)}$$

By steady state error with constant frequency input is
  
$$\lim_{\omega \rightarrow 0} s\phi_c(s) = \frac{\omega_i}{K_0 K_D} = \frac{\omega_i}{\omega_b}$$



SECOND-ORDER PLL.

In this model the constant K_D has units of volts per second because of extra integration.

As the loop transmission magnitude increases, the loop become progressively better damped because an increase in cross over frequency allows more of the zero's positive phase shift of negative phase shift of poles.

For very large loops transmissions, one closed loop pole end up at nearly the frequency of the zero, while the other

Poles heads for infinitely large frequency
 It is straightforward to show that
 Phase transfer function is

$$\frac{\phi_{out}}{\phi_{in}} = \frac{ZzS+1}{(S^2/KDk_0) + ZzS+1}$$

$$\omega_n = \sqrt{KDk_0}$$


$$\xi = \frac{\omega_n Zz}{2} = \frac{Zz \sqrt{KDk_0}}{2}$$

The cross over frequency for loop is

$$\omega_c = \left[\frac{\omega_n^4}{2\omega_z^2} + \omega_n^2 \sqrt{\frac{1}{4} \left(\frac{\omega_n}{\omega_z} \right)^4 + 1} \right]^{1/2}$$

$$\omega_c \approx \frac{\omega_n}{\omega_z}$$


Jitter peaking in second order PLL

 

From Root locus, we see that zero is to right of pole at larger damping ratio hence the closed loop frequency response initially exceeds unity until zero's effect is cancelled by poles.

The frequency rise as starting at zero location and falling cause by first pole. The phase transfer function has magnitude greater than unity above zero frequency until second pole introduces a sufficient roll off.

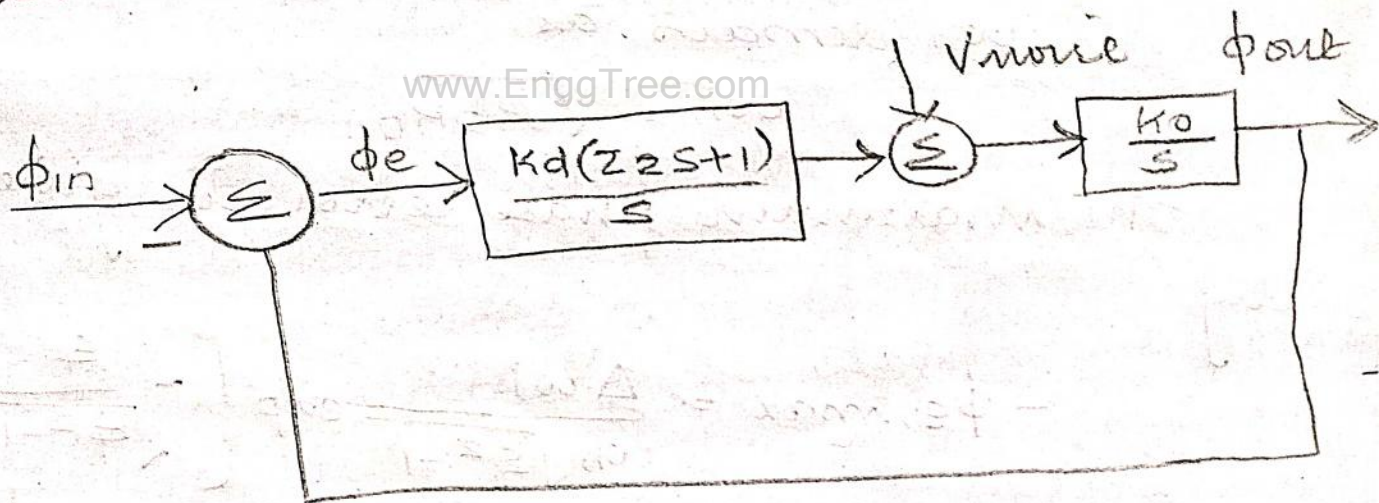SOME NOISE PROPERTIES OF PLL'S.
REJECTION OF VCO DISTURBANCES.



Consider noise as additive at the control port of the VCO. It is a relatively straight forward exercise to show that noise to phase error transfer function is

$$\frac{\phi_e}{V_N} = \frac{SK_0}{s^2 + s z z KDK_0 + KDK_0}$$

Assuming unit step - function noise input inverse laplace - transforming gives us the resulting phase error as function of time.

$$-\phi_E(t) = \frac{\Delta \omega_i}{\omega_n \sqrt{\xi^2 - 1}} \exp(-\xi \omega_n t) \sinh \left(\omega_n \sqrt{\xi^2 - 1} t \right)$$

$\Delta \omega_i$ - initial frequency error due to step function disturbance V_N . The damping ratio ξ of closed loop poles is given by

$$\xi = \frac{\omega_n z}{\omega}$$

ω_n remains as

$$\omega_n = \sqrt{K_D K_O}$$

The maximum phase error is given

by

$$-\phi_{E, \max} = \frac{\Delta \omega_i}{\omega_n \sqrt{\xi^2 - 1}} \exp \left[-\frac{\xi}{\sqrt{\xi^2 - 1}} \tanh^{-1} \frac{\sqrt{\xi^2 - 1}}{\xi} \right]$$

$$\cdot \sinh \left(\tanh^{-1} \frac{\sqrt{\xi^2 - 1}}{\xi} \right)$$

occurs at a time

$$t_{\max} = \frac{1}{\omega_n \sqrt{\xi^2 - 1}} \tanh^{-1} \frac{\sqrt{\xi^2 - 1}}{\xi}$$

$$-\phi_{\epsilon, \max} \approx \frac{\Delta \omega_i}{\omega_c}$$

$$t_{\max} \approx \frac{2 \ln 2 \epsilon}{\omega_c}$$

ω_c is cross-over frequency of loop.

REJECTION OF NOISE ON INPUT.

The bandwidth of PLL helps to minimize the influence of disturbances that alter the VCO frequency.

However, there is a potential drawback to maximizing the bandwidth, above and beyond the stability issues.

As the loop bandwidth increases, the loop gets better at tracking the input. If the input is noise-free, then there is a net improvement overall.

However if the input signal is noisier than the PLL's VCO, then the high-bandwidth loop will faithfully reproduce this input noise at the output.

Hence there is a tradeoff between sensitivity to noise on the input to the loop, and sensitivity to noise that disturbs the VCO frequency.

In general, tuned oscillators are inherently less noisy.

PHASE DETECTORS:

THE ANALOG MULTIPLIER AS A PHASE DETECTOR:


DETECTOR:

In PLLs that have sine-wave inputs and sine wave VCOs, the most common phase detector is the multiplier type and with Gilbert-type topology.

The output of multiplier may be expressed as.

$$AB \cos \omega t \cos(\omega t + \phi) = \frac{AB}{2} [\cos(\phi) - \cos(2\omega t + \phi)]$$

 which is consisting of DC term and double frequency term. For phase detector we are interested only in DC term.



gain 'constant' is a function of phase angle and is given by.

$$K_D = \frac{d}{d\phi} (V_{out}) = -\frac{AB}{2} [\sin(\phi)].$$


- * The output is periodic.
- * The phase detector gain constant is zero when the phase difference is zero and is greatest when the input phase difference is 90° .
- * To maximize the useful phase detection range, the loop should be arranged to lock to a phase difference of 90° and a multiplier is often called as quadrature phase detector.
- * When loop is locked in quadrature the phase detector increase gain by.

$$K_D \Big|_{\phi = \pi/2} = \frac{d}{d\phi} V_{out} \Big|_{\phi = \pi/2} = -\frac{AB}{2}.$$

* Because there are two phase angles the result is zero output from the phase detector; there would be two equilibrium points to which the loop could lock. one of point is stable equilibrium and other is metastable only one corresponds to negative feedback.

THE COMMUTATING MULTIPLIER AS A PHASE DETECTOR

 We assumed in previous cases that both inputs to loop were sinusoidal. Here one of both of inputs may be a square wave.



$$\text{sgn}(x) = 1 \quad \text{if } x > 0$$

$$\text{sgn}(x) = -1 \quad \text{if } x < 0.$$

We assume only the fundamental component of square wave, which is amplitude is $4B/\pi$.

The average output of multiplier is



$$\begin{aligned} \langle V_{out} \rangle &= \frac{4}{\pi} \frac{AB}{2} [\cos(\phi)] \\ &= \frac{2}{\pi} AB [\cos(\phi)]. \end{aligned}$$

The phase detector gain is just $1/\pi$ larger as in sinusoidal case:


$$K_D \Big|_{\phi = \pi/2} = \frac{d}{d\phi} \langle V_{out} \rangle \Big|_{\phi = \pi/2}$$

THE EXCLUSIVE-OR GATE AS A PHASE DETECTOR

 
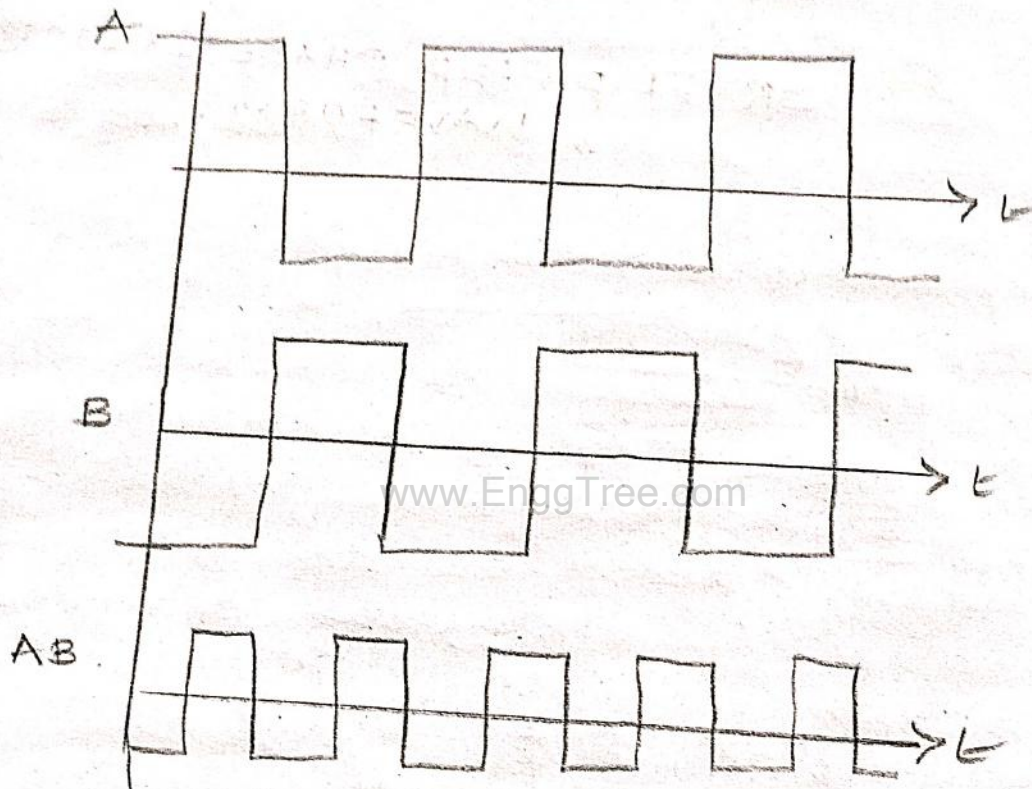
In this case, the two square-wave inputs produce output as we change input phase difference, the output takes the form of square wave of varying duty cycle with 50% duty cycle to a quadrature relationship between the inputs.



SEQUENTIAL PHASE DETECTORS

 



SR FLIP FLOP PHASE DETECTOR WAVEFORM,

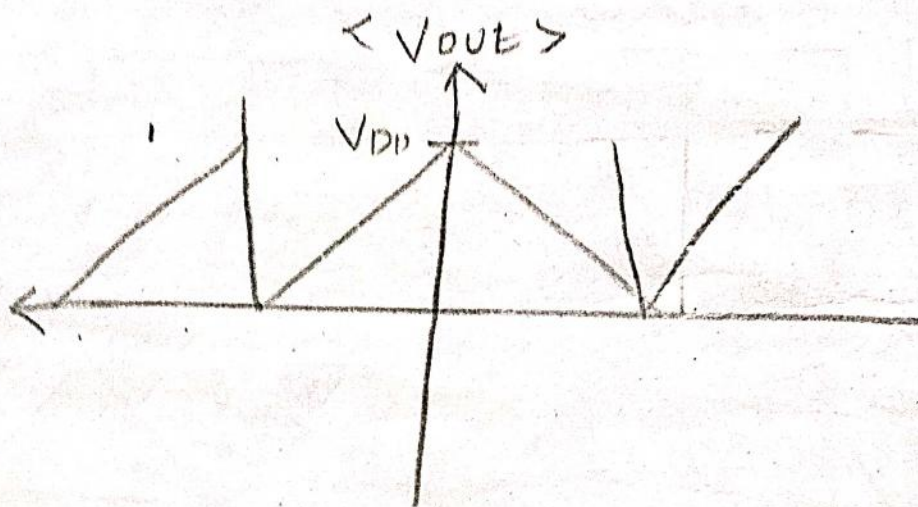 


97
 LOOP FILTERS AND CHARGE PUMPS

LOOP FILTERS:

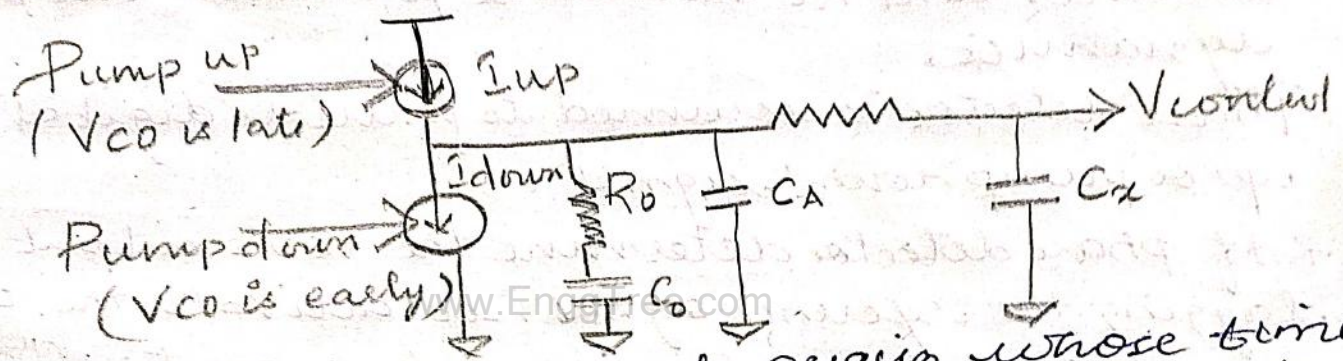 we want to have zero phase error in lock. VCO requires control voltage to produce output of desired frequency, the loop filter must provide an integration. Then to ensure loop stability the loop filter must provide a zero.



- * we have pole and zero at origin whose time constant is R_2C . The value of R_1 is adjusted to provide loop transmission magnitude.
- * A RC network use to correct phase detector with VCO, where static phase error is not zero and loop bandwidth is coupled to static phase error and used only in critical applications.
- * The circuit is used in discrete implementation, but a different approach is used in most IC's.
- * A considerable reduction in complexity and area can be obtained by using an element that is less general-purpose than an op-amp.

 

The popular alter method to op-amp filter is use of charge pump working with RC network where phase detectors control one or more current sources and RC networks provides loop dynamic.

Phase detector is assumed to provide digital 'pump up' or 'pump down' signal.

* If phase detector determine the VCO's output is lagging the reference signal, it activates the top current sources, sending charge to capacitor (pump up). If the VCO is ahead, the bottom current source is activated with drawing charge from capacitor (pump down).

* If there is no Resistor R_o , then we would have pure integration. As usual the series resistor provide loop-stabilizing zero by forcing the high frequency asymptotic impedance to non-zero value. The pump current is given by

$$I = I_{\text{pump}} \frac{\Delta\phi}{2\pi}$$

Transistor M1 and M4 through are different switches operated by up and down commands from phase detector. Depending on state of commands either source current I_{up} or sink


current I_{down} is steered to the output node
 Op. Thus I_{out} equals I_{up} or I_{down} depending on
 phase detector state.

FREQUENCY SYNTHESIZER:

N FREQUENCY SYNTHESIZER

BASIC INTEGER N-SYNTHESIZER

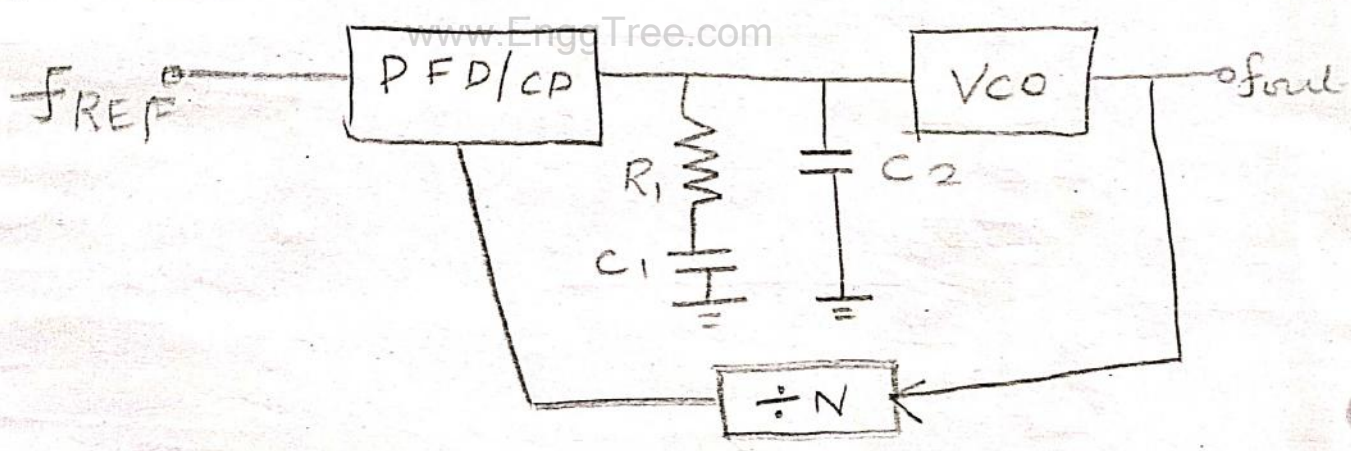Integer-N synthesizers produce an output frequency that is an integer multiple of reference frequency. if N increases by 1, then f_{out} increases by f_{REF} i.e. the minimum channel spacing is equal to the reference frequency.




The divide ratio must be programmable from N_1 to N_2 so that $N_1 f_{REF} = f_1$ and $N_2 f_{REF} = f_2$. We therefore recognize two conditions for the choice of f_{REF} : it must be equal to desired channel spacing and it must be the greatest common divisor of f_1 and f_2 . The choice may be dominated by one of two conditions

Eg: the minimum channel spacing may be smaller than the greatest common divisor of f_1 and f_2 .

5th sem
Priority

The simplicity of integer-N synthesizer makes an attractive choice. Behaving as a standard PLL.

DIRECT DIGITAL FREQUENCY SYNTHESIZER

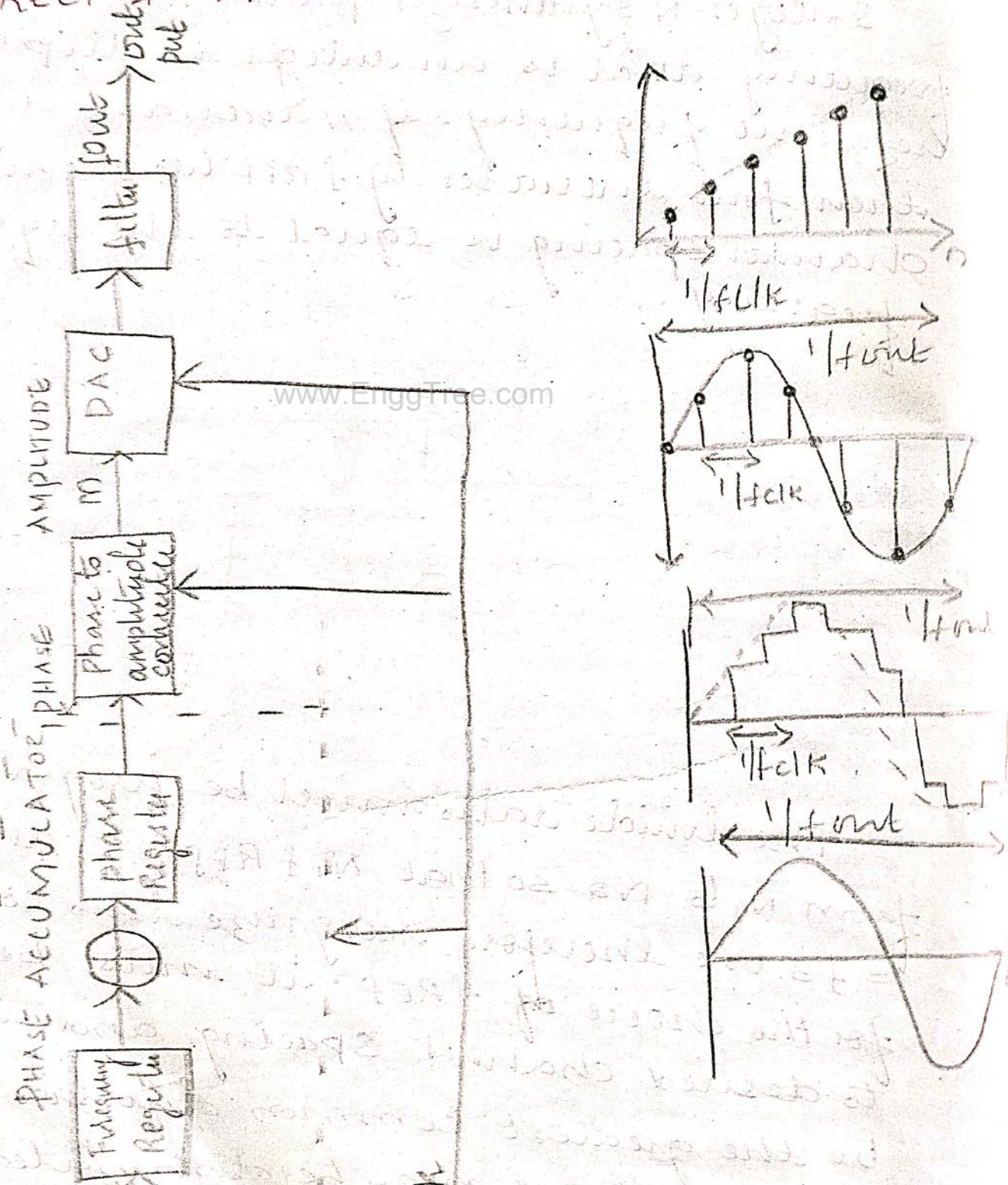

- * DDFS is a method of producing an analog waveform usually a sine wave by generating a time varying signal in digital form and then performing a digital to analog conversion.
- * The operations within DDFS device are primarily digital, therefore it can offer fast switches between output frequencies, fine frequency resolution and operation over a broad spectrum of frequencies.
- * The digital frequency synthesizer employs a stable frequency reference clock to define times at which digital sinusoidal sample values are produced.
- * These samples are converted from digital to analog format and smoothed by reconstruction filter to produce analog frequency signal.
- * A DDFS consists of Phase Accumulator and a sine lookup table.
- * The input to phase accumulator is frequency control word, which determines the periodicity of phase accumulator.
- * The PA is updated to frequency word or tuning word at each clock.

The output is fed to LUT then converted to analog signal using DAC.

www.EnggTree.com